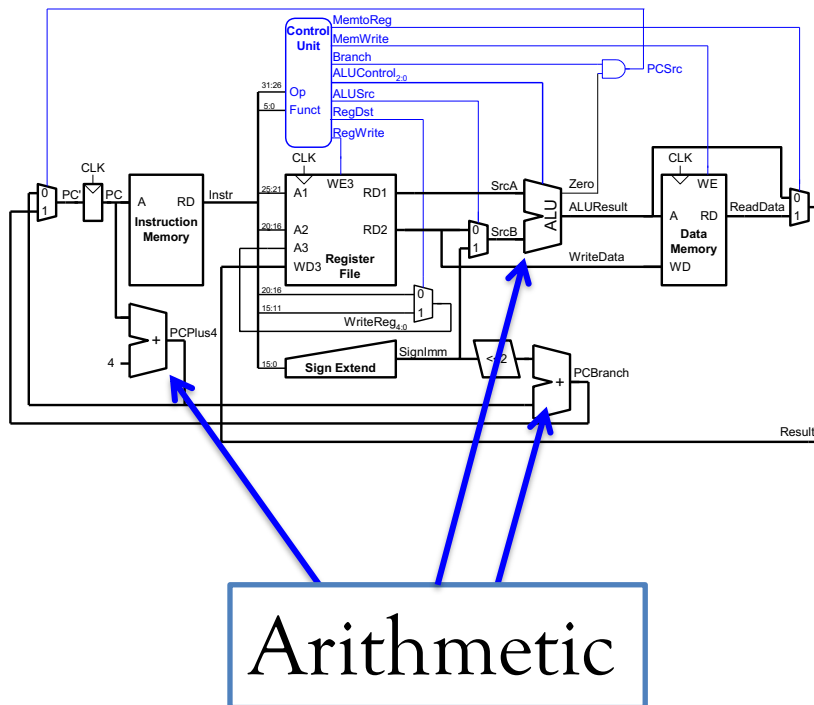


Arithmetic Circuits: Subtractors, Multipliers, ALU

Becker/Molitor, Chapter 9.2+9.3

Jan Reineke
Universität des Saarlandes

Roadmap: Computer architecture



1. Combinatorial circuits: Boolean Algebra/Functions/Expressions/Synthesis
2. Number representations
3. Arithmetic Circuits:
Addition, **Multiplication, Division, ALU**
4. Sequential circuits: Flip-Flops, Registers, SRAM, Moore and Mealy automata
5. Verilog
6. Instruction Set Architecture
7. Data path & Control path
8. Performance: RISC vs. CISC, Pipelining, Memory Hierarchy

Subtraction

As we have $-[b] = [\bar{b}] + 1$ the difference $[a] - [b]$ is equal to the sum $[a] + [\bar{b}] + 1$.

- Derive subtractor circuit from adder circuit
- combined adder/subtractor

Reminder: Two's complement

Lemma:

Let d be a fixed-point number and \bar{d} the number obtained by flipping all bits ($0 \rightarrow 1$, $1 \rightarrow 0$) in d .

Then: $[\bar{d}]_2 + 1 = -[d]_2$.

Example: $n = 2$, $k = 0$:

d	000	001	010	011	100	101	110	111
$[d]_2$	0	1	2	3	-4	-3	-2	-1

Example: Subtraction


$$[a]_2 = [0110]_2 = 6_{10}$$

$$[b]_2 = [0111]_2 = 7_{10}$$


$$[\bar{b}]_2 = [1000]_2 = -8_{10}$$

0	1	1	0
1	0	0	0
			1
<hr/>			
1	1	1	1
$= (-1)_{10}$			

Schematic of a subtractor

 

Schematic of a combined adder/subtractor

 

$$b_i \oplus 0 = b_i$$

$$b_i \oplus 1 = \overline{b_i}$$

$$sub = 0: [a]_2 + [b]_2 + 0$$

$$sub = 1: [a]_2 + [\overline{b}]_2 + 1 = [a]_2 - [b]_2$$

Multipliers

Wanted: Circuit for the **multiplication** of two binary numbers $\langle a_{n-1}, \dots, a_0 \rangle$, $\langle b_{n-1}, \dots, b_0 \rangle$.

Example:

$$(110) \cdot (101) \\ = 6_{10} \cdot 5_{10}$$

$$\begin{array}{r} 110 \\ 000 \\ \hline 11010 \end{array}$$

$$= 30_{10}$$

Outputs of a multipliers

How many bits are required for the result?

$$\langle a \rangle \cdot \langle b \rangle \leq$$

$$(2^n - 1) \cdot (2^n - 1) = 2^{2n} - 2^{n+1} + 1 \leq 2^{2n} - 1$$

*Thus: **2n bits** are sufficient to represent the product of two n-bit binary numbers.*

Multipliers

Definition: An **n-bit multiplier** is a circuit that computes the following function:

$mul_n: \mathbf{B}^{2n} \rightarrow \mathbf{B}^{2n}$ with

$mul_n(a_{n-1}, \dots, a_0, b_{n-1}, \dots, b_0) = (p_{2n-1}, \dots, p_0)$ with


$\langle p_{2n-1}, \dots, p_0 \rangle = \langle a \rangle \cdot \langle b \rangle$

$$\langle a \rangle \cdot \langle b \rangle \stackrel{\text{Def. } \langle \cdot \rangle}{=} \langle a \rangle \cdot \sum_{i=0}^{n-1} b_i \cdot 2^i = \sum_{i=0}^{n-1} \underbrace{\langle a \rangle \cdot b_i \cdot 2^i}_{\text{partial product}}$$

The multiplication matrix

n partial products, each with $2n$ bits

$$\begin{pmatrix} pp_0 \\ pp_1 \\ \vdots \\ pp_{n-1} \end{pmatrix} = \begin{pmatrix} 0 & 0 & \dots & 0 & 0 & a_{n-1}b_0 & a_{n-2}b_0 & \dots & a_1b_0 & a_0b_0 \\ 0 & 0 & \dots & 0 & a_{n-1}b_1 & a_{n-2}b_1 & a_{n-3}b_1 & \dots & a_0b_1 & 0 \\ \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots \\ 0 & a_{n-1}b_{n-1} & \dots & a_2b_{n-1} & a_1b_{n-1} & a_0b_{n-1} & 0 & \dots & 0 & 0 \end{pmatrix}$$

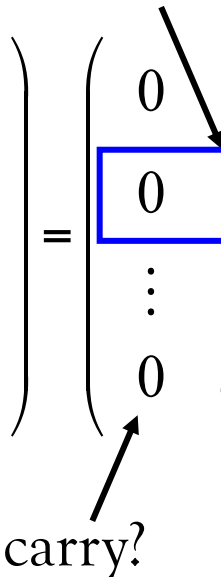

Implementation of the mult. matrix?

→ with n^2 AND gates

(and n^2 constants 0).

Fast addition of partial products

Goal: Fast addition of **n partial products** of length $2n$.


First approach:

Use carry-lookahead adders (CLAs).

Cost: $O(n^2)$

Depth:

 
- $O(n \cdot \log n)$ if partial products are summed up one by one linearly
- $O(\log^2 n)$ ($= O((\log n)^2)$) for tree-shaped summation of partial products



Brainstorming:

Addition of partial products:

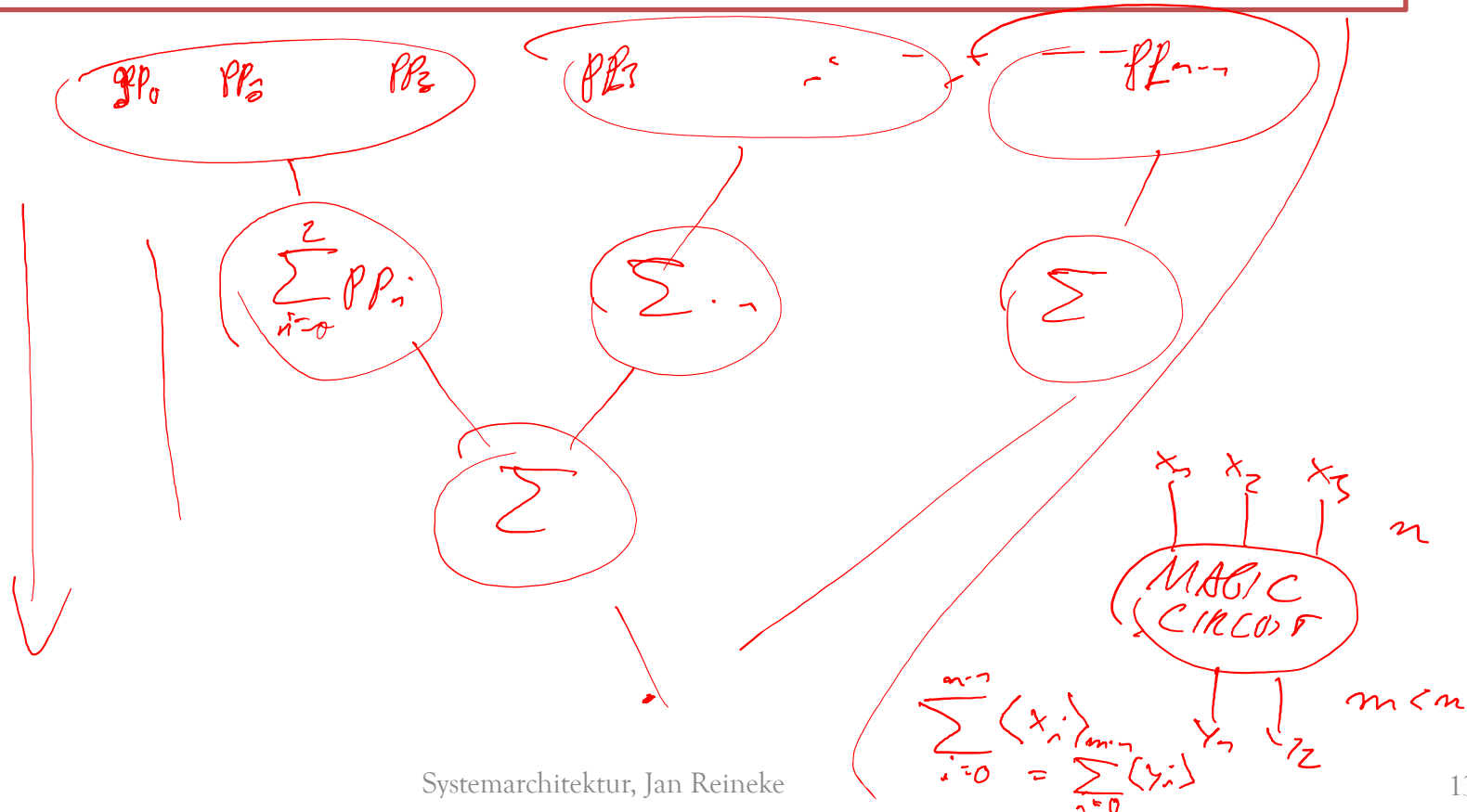Can we do better than adding up the partial products in $O(\log^2 n)$?



Fast addition of **n partial products**


Use **carry-save adders**.

Reduction of three input values **u**, **v**, **w** into two output values **s**, **c** s.t. $\langle u \rangle + \langle v \rangle + \langle w \rangle = \langle s \rangle + \langle c \rangle$.

u_{n-1}	u_{n-2}	\dots	u_2	u_1	u_0
v_{n-1}	v_{n-2}		v_2	v_1	v_0
w_{n-1}	w_{n-2}		w_2	w_1	w_0
c_{n-1}	c_{n-2}	c_{n-3}	\dots	c_1	c_0
0	s_{n-1}	s_{n-2}		s_2	s_1
				s_0	

Solved by juxtaposition of independent full adders (**not** in a chain!)

Carry-save adder (also: 3:2 adder)

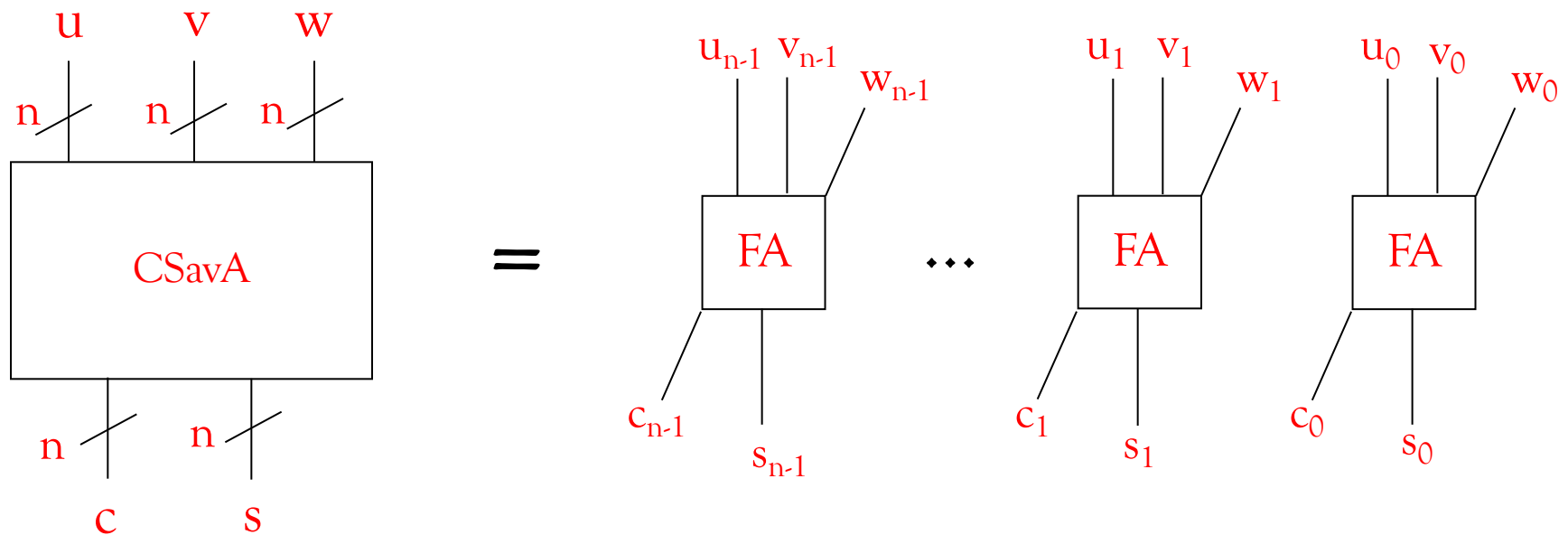


Cost: $C(\text{CSavA}^n) = n \cdot C(\text{FA}) = 5 \cdot n$

Depth: $\text{depth}(\text{CSavA}^n) = \text{depth}(\text{FA}) = 3$

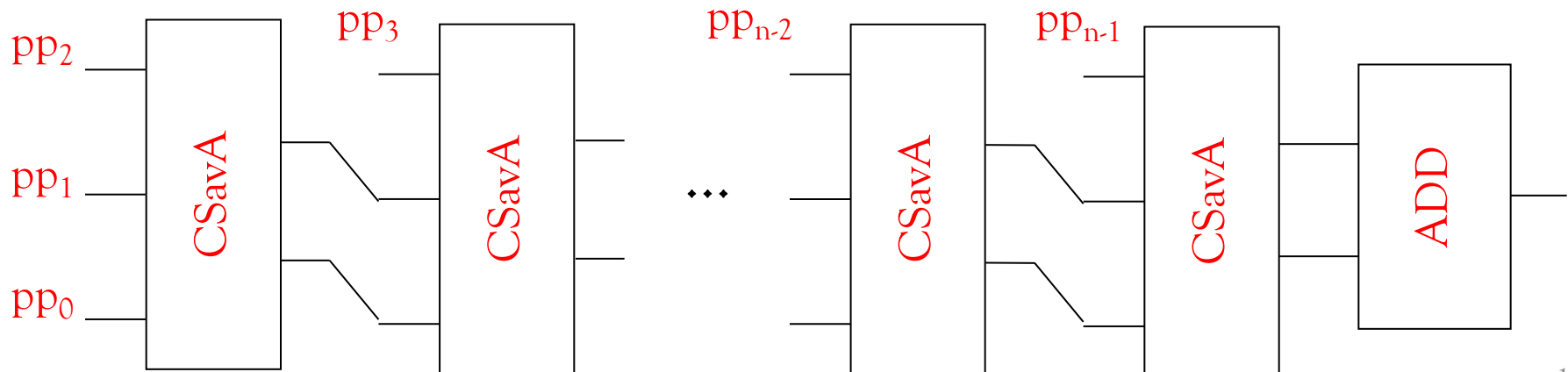1. Serial solution

- Cascade connection of $n-2$ CSavAs of length $2n$:
 - Combine n partial products into two $2n$ -bit words
- Add the last two $2n$ -bit words using a CLA
- Cost: $O(n^2)$, Depth: $O(n)$




2. Tree-shaped solution


- Combine two carry-save adders to reduce **four $2n$ -bit input words** into two output words: 4-to-2 reducer
- Balanced binary tree of **4-to-2 reducers** to summarize the n partial products using two $2n$ -bit words
- Addition of the two final $2n$ -bit words using a CLA

Cost: $O(n^2)$

Depth: $O(\log n)$

 

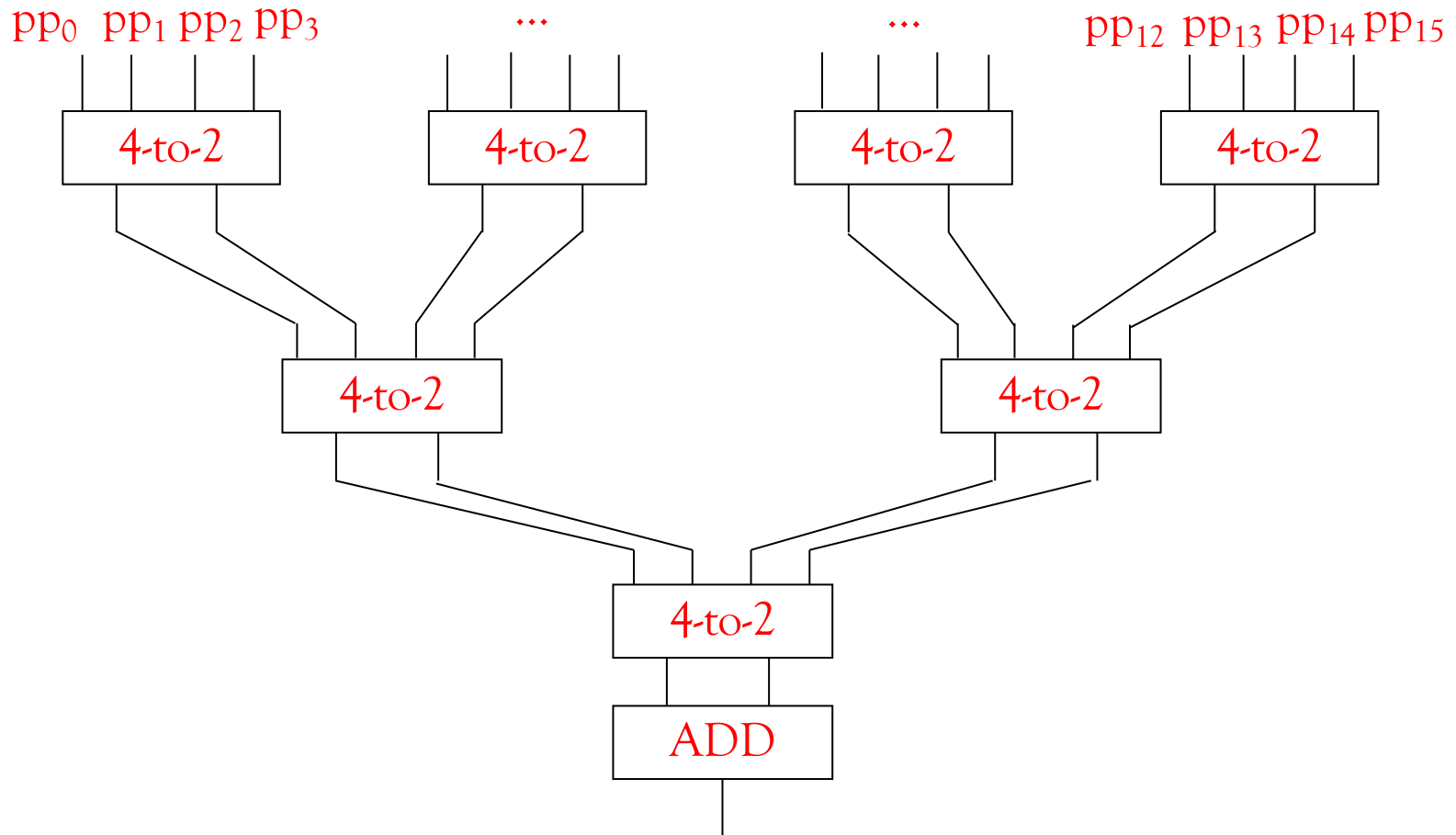Adder stage of the log-time multiplier for 16 bits




Construction of an ALU

ALU = arithmetic logic unit for performing basic arithmetic and logic operations

Here: n -bit-ALU with:

- 2 n -bit operands a , b , carry-in c
- m -bit select input, which selects the function to execute
- $(n+1)$ -bit output

Schematic of an n-bit ALU

 

Example ALU specification

Here: 8 functions, i.e. 3-bit select input

Function number			ALU function
s_2	s_1	s_0	
0	0	0	$0 \dots 0$
0	0	1	$[b] - [a]$
0	1	0	$[a] - [b]$
0	1	1	$[a] + [b] + c$
1	0	0	$a \oplus b = (a_{n-1} \oplus b_{n-1}, \dots, a_0 \oplus b_0)$
1	0	1	$a \vee b = (a_{n-1} \vee b_{n-1}, \dots, a_0 \vee b_0)$
1	1	0	$a \wedge b = (a_{n-1} \wedge b_{n-1}, \dots, a_0 \wedge b_0)$
1	1	1	$1 \dots 1$

„Arithmetic“

„Logic“

Possible implementations of an ALU

1. Possibility:

Implement f_0, \dots, f_{2^m-1} separately via circuits C_i for f_i ; then select correct output via generalized multiplexer


(see upcoming figure)

2. Possibility:


Shared circuit for similar functions

(see upcoming figure)

1. Possible implementation

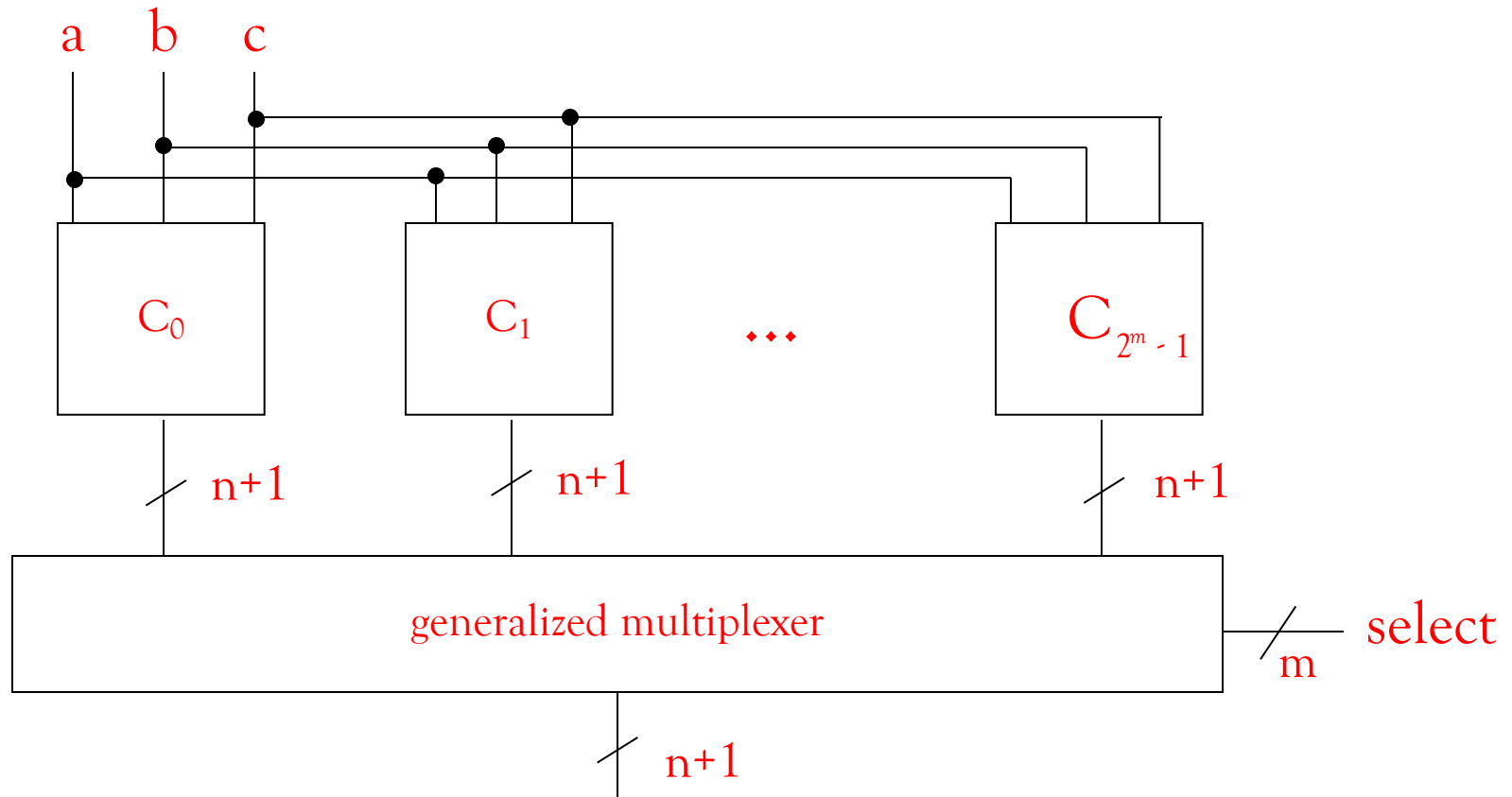

2. Possible implementation

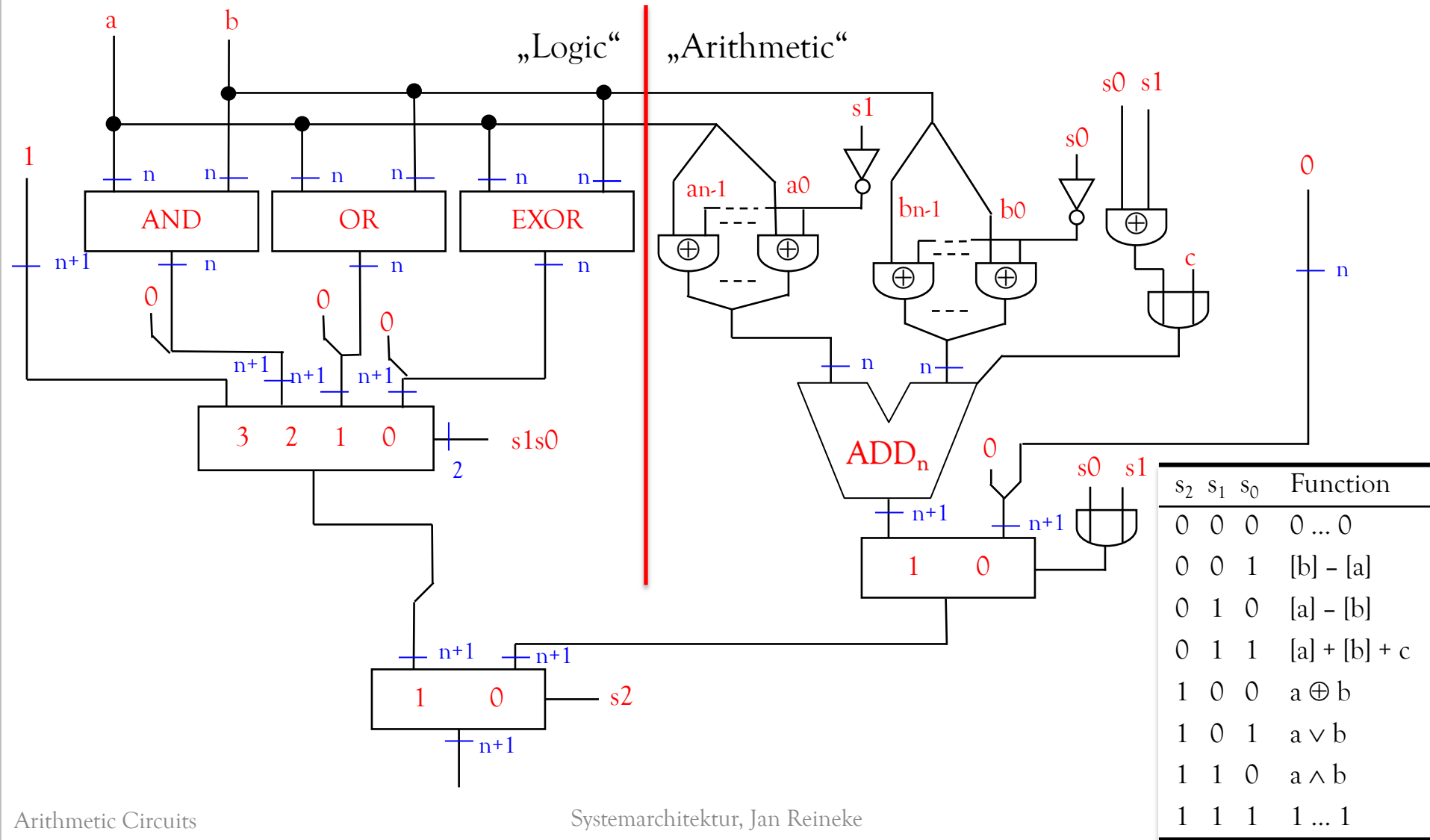

Outlook:

Datapath and instruction execution

