

## Systemarchitektur SS 2021

### Lösungsskizze 4

#### Aufgabe 4.1: Abhängigkeitsbegriff

1. Im Folgenden werden wir mit  $x_i$  (wobei  $1 \leq i \leq N$ ) das  $i$ -te element eines Tupels  $x \in \mathbb{B}^N$  bezeichnen.

$$dep_f := \{(i, j) \mid \exists x, y \in \mathbb{B}^n : (f(x)_j \neq f(y)_j) \wedge (\forall i' : (i' \neq i) \Rightarrow (x_{i'} = y_{i'}))\}$$

- 2.

$x_1$	$x_2$	$s_1$	$s_2$
0	0	0	0
0	1	0	0
1	0	1	0
1	1	1	0

#### Aufgabe 4.2: Inkrementierer

1. Die rekursive Definition eines  $n$ -Inkrementierers ist in Abbildung 1 gezeigt<sup>1</sup>.

2. Beweis durch Induktion über  $n \in \mathbb{N}_+$ :

- Induktionsanfang:  $n = 1 \Rightarrow a = a_0$ :  
 $Inc_1$  ist ein Halbaddierer, der als Eingabe  $(a_0, c_0)$  hat. Ein Halbaddierer ist korrekt.  $\Rightarrow$  Für die Ausgabe  $s$  gilt  $\langle s = \langle c_1, s_0 \rangle = \langle a_0 \rangle + c_0$ .
- Induktionsvoraussetzung: Die Aussage sei für ein beliebiges aber festes  $n \in \mathbb{N}_+$  gezeigt.
- Induktionsschritt:  $n - 1 \rightarrow n$   
 Eingabe an  $Inc_n$ :  $(a_{n-1}, \dots, a_0)$   
 Zeige für Ausgabe  $(s_n, s_{n-1}, \dots, s_0)$  gilt:  
 $\langle s \rangle = \langle c_n, s_{n-1}, \dots, s_0 \rangle = \langle a_{n-1}, \dots, a_0 \rangle + c_0$ .

$$\begin{aligned}
 \langle c_n, s_{n-1}, \dots, s_0 \rangle &= 2^{n-1} \langle c_n, s_{n-1} \rangle + \langle s_{n-2}, \dots, s_0 \rangle \\
 &= 2^{n-1} \cdot (\langle a_{n-1} \rangle + \langle c_{n-1} \rangle) + \langle s_{n-2}, \dots, s_0 \rangle && \text{(Halbaddierer)} \\
 &= 2^{n-1} \langle a_{n-1} \rangle + \langle c_{n-1}, s_{n-2}, \dots, s_0 \rangle \\
 &= 2^{n-1} \langle a_{n-1} \rangle + \langle a_{n-2}, \dots, a_0 \rangle + \langle c_0 \rangle && \text{(I.V.)} \\
 &= \langle a_{n-1}, \dots, a_0 \rangle + \langle c_0 \rangle
 \end{aligned}$$

■

3. Die Kosten und Tiefe sind:

$$C(Inc_1) = C(HA) = 2, \quad C(Inc_n) = C(HA) + C(Inc_{n-1})$$

$$D(Inc_1) = D(HA) = 1, \quad D(Inc_n) = D(HA) + D(Inc_{n-1})$$

<sup>1</sup>Entnommen aus W. J. Paul: Sysbook, SS 2013

4. •  $C(Inc_n) = C(HA) * n = 2n$   
 Beweis durch Induktion über  $n$ .  
 IA:  $n = 1$

$$C(Inc_1) = C(HA) = 2 = 2 * 1 = 2n$$

IV:

Für beliebiges aber festes  $n \in \mathbb{N} : C(Inc_n) = 2n$

IS:  $n \rightarrow n+1$

$$C(Inc_{n+1}) = C(HA) + C(Inc_n) \stackrel{IV}{=} C(HA) + 2n = 2 + 2n = 2(n+1)$$

■

- $D(Inc_n) = D(HA) * n = n$   
 Beweis durch Induktion über  $n$ .  
 IA:  $n = 1$

$$D(Inc_1) = D(HA) = 1 = n$$

IV:


Für beliebiges aber festes  $n \in \mathbb{N} : D(Inc_n) = n$

IS:  $n \rightarrow n+1$

$$D(Inc_{n+1}) = D(HA) + D(Inc_n) \stackrel{IV}{=} D(HA) + n = 1 + n = (n+1)$$

■

$n = 1$ :

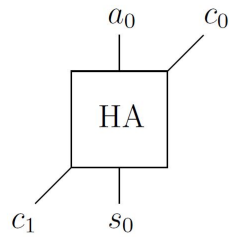

$n > 1$ :


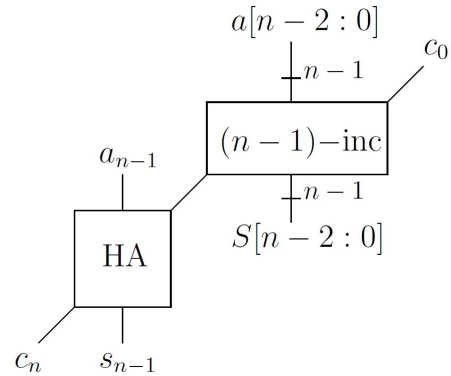



Abbildung 1:  $n$ -Inkrementierer

### Aufgabe 4.3: Modellierung durch Schaltkreise

(a) Konstruktion:

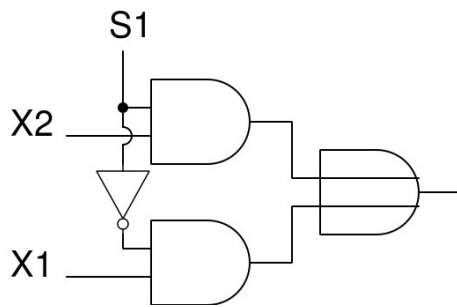

(b) Konstruktion:

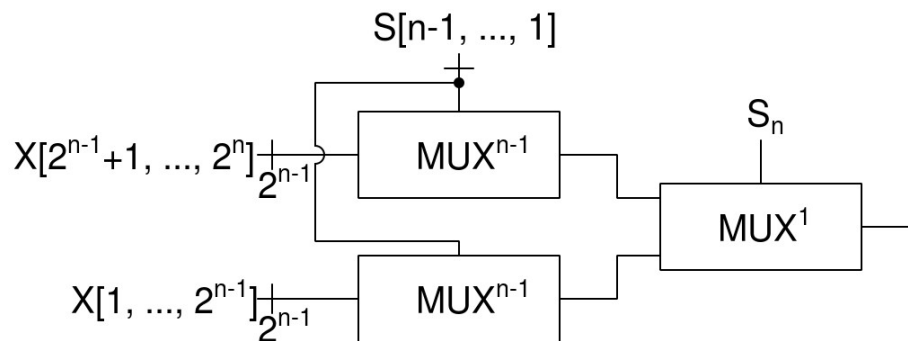

(c) Ein so konstruierter  $\text{MUX}^n$  hat die Tiefe  $3 + 2(n - 1) = 2n + 1$  und besteht aus  $2^n - 1$  einfachen MUXen.

## System Architecture SS 2021

### Solution Sketch 4

#### Problem 4.1: Notion of Dependency

1. In the following, we will use  $x_i$  (with  $1 \leq i \leq N$ ) to refer to the  $i$ -th element of a tuple  $x \in \mathbb{B}^N$ .

$$dep_f := \{(i, j) \mid \exists x, y \in \mathbb{B}^n : (f(x)_j \neq f(y)_j) \wedge (\forall i' : (i' \neq i) \Rightarrow (x_{i'} = y_{i'}))\}$$

- 2.

$x_1$	$x_2$	$s_1$	$s_2$
0	0	0	0
0	1	0	0
1	0	1	0
1	1	1	0

#### Problem 4.2: Incrementer

1. The recursive definition of an  $n$ -bit incrementer is shown in Figure 2<sup>2</sup>.
2. Proof by induction on  $n \in \mathbb{N}_+$ :
  - Base case:  $n = 1 \Rightarrow a = a_0$ :  
 $Inc_1$  is a half adder which has as input  $(a_0, c_0)$ . A half adder is correct. Thus, for the output  $s$  we have  $\langle s \rangle = \langle c_1, s_0 \rangle = \langle a_0 \rangle + c_0$ .
  - Induction hypothesis (IH): The statement holds for an arbitrary but fixed  $n \in \mathbb{N}_+$ .
  - Induction step:  $n - 1 \rightarrow n$   
 Input for  $Inc_n$ :  $(a_{n-1}, \dots, a_0)$   
 We have to show that for the output  $s = c_n s_{n-1} \dots s_0$  the following holds:  
 $\langle s \rangle = \langle c_n, s_{n-1}, \dots, s_0 \rangle = \langle a_{n-1}, \dots, a_0 \rangle + c_0$ .

$$\begin{aligned}
 \langle c_n, s_{n-1}, \dots, s_0 \rangle &= 2^{n-1} \langle c_n, s_{n-1} \rangle + \langle s_{n-2}, \dots, s_0 \rangle \\
 &= 2^{n-1} \cdot (\langle a_{n-1} \rangle + \langle c_{n-1} \rangle) + \langle s_{n-2}, \dots, s_0 \rangle && \text{(Half adder)} \\
 &= 2^{n-1} \langle a_{n-1} \rangle + \langle c_{n-1}, s_{n-2}, \dots, s_0 \rangle \\
 &= 2^{n-1} \langle a_{n-1} \rangle + \langle a_{n-2}, \dots, a_0 \rangle + \langle c_0 \rangle && \text{(IH)} \\
 &= \langle a_{n-1}, \dots, a_0 \rangle + \langle c_0 \rangle
 \end{aligned}$$

■

3. The cost and depth are:

$$C(Inc_1) = C(HA) = 2, \quad C(Inc_n) = C(HA) + C(Inc_{n-1})$$

$$D(Inc_1) = D(HA) = 1, \quad D(Inc_n) = D(HA) + D(Inc_{n-1})$$

<sup>2</sup>Taken from W. J. Paul: Sysbook, SS 2013

4. •  $C(Inc_n) = C(HA) * n = 2n$   
 Proof by induction on  $n$ .  
 Base case:  $n = 1$

$$C(Inc_1) = C(HA) = 2 = 2 * 1 = 2n$$

Induction hypothesis (IH):

For an arbitrary but fixed  $n \in \mathbb{N} : C(Inc_n) = 2n$

Induction step:  $n \rightarrow n+1$

$$C(Inc_{n+1}) = C(HA) + C(Inc_n) \stackrel{IH}{=} C(HA) + 2n = 2 + 2n = 2(n+1)$$

■

- $D(Inc_n) = D(HA) * n = n$   
 Proof by induction on  $n$ .  
 Base case:  $n = 1$

$$D(Inc_1) = D(HA) = 1 = n$$

Induction hypothesis (IH):


For an arbitrary but fixed  $n \in \mathbb{N} : D(Inc_n) = n$

Induction step:  $n \rightarrow n+1$

$$D(Inc_{n+1}) = D(HA) + D(Inc_n) \stackrel{IH}{=} D(HA) + n = 1 + n = (n+1)$$

■

$n = 1$ :

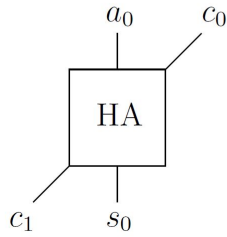

$n > 1$ :


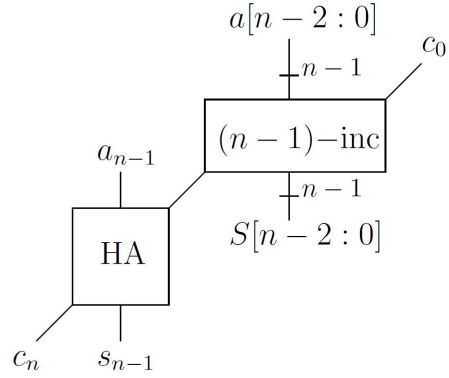



Figure 2:  $n$ -bit incrementer

### Problem 4.3: Modeling Through Circuits

(a) Construction:

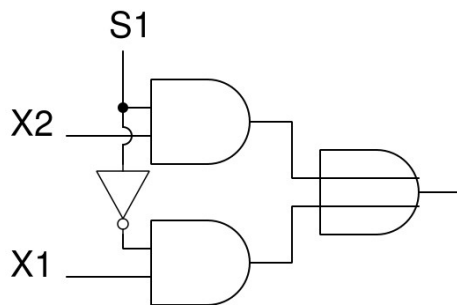

(b) Construction:

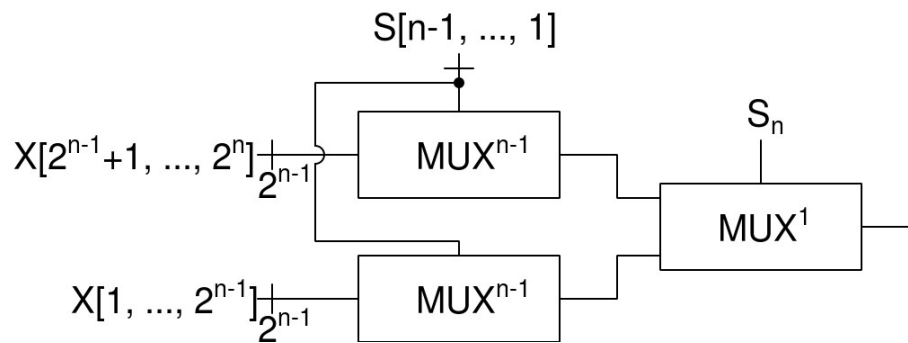

(c) A  $\text{MUX}^n$  constructed in this way has depth  $3 + 2(n - 1) = 2n + 1$  and consists of  $2^n - 1$  simple MUXes.