

Hardware Description Languages: Verilog

Jan Reineke




UNIVERSITÄT
DES
SAARLANDES

Step I: circuit design

- manual with paper and pencil
- at the level of individual transistors

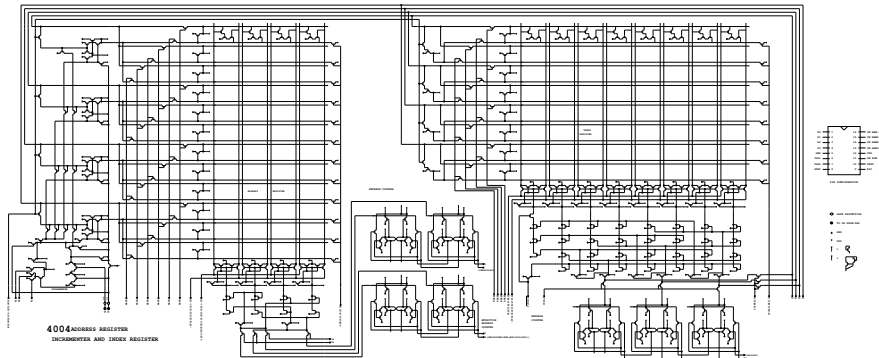Example: Intel 4004, 2.300 transistors, 108KHz, $10\mu m$ (excerpt)
first mass-produced single-chip microprocessor!



<http://www.4004.com/assets/redrawn-4004-schematics-2006-11-12.pdf>
Re-drawn schematics based on Revision G of the original Intel 4004 schematics by Intel Corporation (August 6, 1976). Schematic capture and design verification by Fred Huettig, Brian Silverman and Barry Silverman (February 2, 2006).

Step I: circuit design

- manual with paper and pencil
- at the level of individual transistors

Step II: Fabrication of photomasks for lithographic process

- manual labor
- error prone

History: Hardware design in 1970



Photo courtesy of the Intel Corporation, as published on
<http://www.computerhistory.org/revolution/digital-logic/12/287/1614>

Hardware description languages

- Abstract from transistors
- Simulation
- Hardware synthesis
 - using computer-aided design (CAD) programs
 - ▶ Field Programmable Gate Array (FPGA)
 - ▶ Application-Specific Integrated Circuit (ASIC)

Hardware description languages

- Abstract from transistors
- Simulation
- Hardware synthesis
 - using computer-aided design (CAD) programs
 - ▶ Field Programmable Gate Array (FPGA)
 - ▶ Application-Specific Integrated Circuit (ASIC)

In this course, we use ...

Verilog, originally developed by Gateway Design Automation in 1984

Other languages: VHDL, SystemVerilog, Chisel

Previous concepts in the course

Previous concepts in the course

Boolean functions $\mathbb{B}^n \rightarrow \mathbb{B}^m$

Boolean expressions $a \wedge b$

Combinatorial circuits

Previous concepts in the course

Boolean functions $\mathbb{B}^n \rightarrow \mathbb{B}^m$

Boolean expressions $a \wedge b$

Combinatorial circuits

Moore/Mealy automata

Memory elements (Flip-Flops, SRAM, ...)

Sequential circuits

1 Introduction


2 Verilog for Hardware Synthesis

- Combinatorial circuits
- Sequential circuits

3 Simulation

- Test benches

4 *Optional:* FPGA and Synthesis

 

```
module name(  
    input a,  
    input [1:0] b,  
    input c,  
    output y  
);  
  
    // functionality  
  
endmodule
```

Assignments and Bitwise operators

- Assignment of signals via `assign` and `=`
- Bitwise operators correspond to gates
And `&`, Or `|`, Negation `~`, Xor `^`

Example: Half adder

Assignments and Bitwise operators

- Assignment of signals via `assign` and `=`
- Bitwise operators correspond to gates
And `&`, Or `|`, Negation `~`, Xor `^`

Example: Half adder

```
module halfadder(  
    input a,  
    input b,  
    output s,  
    output c  
);
```

```
endmodule
```

Assignments and Bitwise operators

- Assignment of signals via `assign` and `=`
- Bitwise operators correspond to gates
And `&`, Or `|`, Negation `~`, Xor `^`

Example: Half adder

```
module halfadder(  
    input a,  
    input b,  
    output s,  
    output c  
);  
    assign s = a ^ b;  
    assign c = a & b;  
endmodule
```

- General form $N'Bw$
 - ▶ N number of bits
 - ▶ B basis of the numeral system
 - ▶ w sequence of numerals (digits)

■ General form $N'Bw$

- ▶ N number of bits (*independently* (!) of the employed numeral system)
- ▶ B basis of the numeral system
- ▶ w sequence of numerals (digits)

■ General form $N'Bw$

- ▶ N number of bits (*independently* (!) of the employed numeral system)
- ▶ B basis of the numeral system
- ▶ w sequence of numerals (digits)

■ Examples:

- ▶ binary numbers 4' b1011
- ▶ long binary numbers 8' b1010_0011
- ▶ *without* number of bits ' b101
- ▶ decimal 4' d5
- ▶ hexadecimal 8' ha3
- ▶ signed decimal number -3' sd5 (s for “signed”)

■ General form $N'Bw$

- ▶ N number of bits (*independently* (!) of the employed numeral system)
- ▶ B basis of the numeral system
- ▶ w sequence of numerals (digits)

■ Examples:

- ▶ binary numbers 4' b1011
- ▶ long binary numbers 8' b1010_0011
- ▶ *without* number of bits ' b101
- ▶ decimal 4' d5
- ▶ hexadecimal 8' ha3
- ▶ signed decimal number -3' sd5 (s for “signed”)

■ Don't-care values 3' b1xx (e.g. irrelevant signals in the MIPS decoder)

- ▶ Simulation: simplifies debugging
- ▶ Synthesis: more flexibility

Comparison and selection operators

- bit-by-bit (in)equality `==`, `!=`
- unsigned comparison of values `<`, `<=`, ...
- ternary operator `a ? b : c`

Example: 4-bit multiplexer

Comparison and selection operators

- bit-by-bit (in)equality `==`, `!=`
- unsigned comparison of values `<`, `<=`, ...
- ternary operator `a ? b : c`

Example: 4-bit multiplexer

```
module multiplexer(  
    input s,  
    input [3:0] x0,  
    input [3:0] x1,  
    output [3:0] y  
);  
  
endmodule
```

Comparison and selection operators

- bit-by-bit (in)equality `==`, `!=`
- unsigned comparison of values `<`, `<=`, ...
- ternary operator `a ? b : c`

Example: 4-bit multiplexer


```
module multiplexer(  
    input s,  
    input [3:0] x0,  
    input [3:0] x1,  
    output [3:0] y  
);  
    assign y = (s == 1'b0) ? x0 : x1;  
endmodule
```

Instantiating modules

```
modulename instancename (  
    .param1name (arg1name) ,  
    .param2name (arg2name) ,  
    ...  
);
```

Temporary signals via `wire`


Example: Full adder

 

Example: Full adder

```
module fulladder(  
    input a0,  
    input b0,  
    input c,  
    output s0,  
    output s1  
);
```


```
endmodule
```

 

Example: Full adder


```
module fulladder(  
    input a0,  
    input b0,  
    input c,  
    output s0,  
    output s1  
);  
    wire ha0c, ha0s, ha1c;
```

```
endmodule
```

 

 
Example: Full adder

```
module fulladder(  
    input a0,  
    input b0,  
    input c,  
    output s0,  
    output s1  
);  
    wire ha0c, ha0s, ha1c;  
    halfadder ha0(.a(a0), .b(b0), .c(ha0c), .s(ha0s));  
  
endmodule
```



 
Example: Full adder

```
module fulladder(  
    input a0,  
    input b0,  
    input c,  
    output s0,  
    output s1  
);  
    wire ha0c, ha0s, ha1c;  
    halfadder ha0(.a(a0), .b(b0), .c(ha0c), .s(ha0s));  
    halfadder ha1(.a(ha0s), .b(c), .c(ha1c), .s(s0));  
endmodule
```



Example: Full adder

```
module fulladder(  
    input a0,  
    input b0,  
    input c,  
    output s0,  
    output s1  
);  
    wire ha0c, ha0s, ha1c;  
    halfadder ha0(.a(a0), .b(b0), .c(ha0c), .s(ha0s));  
    halfadder ha1(.a(ha0s), .b(c), .c(ha1c), .s(s0));  
    assign s1 = ha0c | ha1c;  
endmodule
```

 

- Part-selects of `a[7:0]`

`a[2] or a[1:0] or a[3+: 4] (= a[6:3])`

- Part-selects of $a[7:0]$
 $a[2]$ or $a[1:0]$ or $a[3+:4]$ ($= a[6:3]$)
- If e.g. $a[7:0] = 10011011$
Then $a[2] = 0$, $a[1:0] = 11$, and $a[6:3] = 0011$.

- Shift operation, logical (fills with zero) \ll , \gg

E.g. $1010 \gg 1 = 0101$

- Shift operation, logical (fills with zero) \ll, \gg
E.g. $1010 \gg 1 = 0101$
- Shift operation, arithmetic (keep sign) \lll, \ggg
E.g. $1010 \ggg 1 = 1101$

- Shift operation, logical (fills with zero) \ll , \gg
E.g. $1010 \gg 1 = 0101$
- Shift operation, arithmetic (keep sign) \lll , \ggg
E.g. $1010 \ggg 1 = 1101$
- In practice, \lll and \ll behave the same.

- Reduction $\&a$ of $a[7:0]$
is equivalent to $a[7] \& a[6] \& \dots \& a[0]$

- Reduction $\&a$ of $a[7:0]$
is equivalent to $a[7] \& a[6] \& \dots \& a[0]$
- arithmetic operators (unsigned) $+$, $*$, \dots

- Reduction `&a` of `a[7:0]`
is equivalent to `a[7] & a[6] & ... & a[0]`
- arithmetic operators (unsigned) `+`, `*`, ...
- Concatenation of `a` and `b` into `c[1:0]`
`assign c[1:0] = {a, b};`

- Reduction & a of $a[7:0]$
is equivalent to $a[7] \& a[6] \& \dots \& a[0]$
- arithmetic operators (unsigned) $+$, $*$, \dots
- Concatenation of a and b into $c[1:0]$
`assign c[1:0] = {a, b};`
- Duplication of bits $c[31:0] = \{16\{2'b10\}\}$
 $= c[31:0] = 10$

1 Introduction

2 Verilog for Hardware Synthesis

- Combinatorial circuits
- Sequential circuits

3 Simulation

- Test benches

4 *Optional:* FPGA and Synthesis

Two types of memories:

- level-triggered latches
- edge-triggered flip-flops

Two types of memories:

- level-triggered latches
- edge-triggered flip-flops

Both types of memory are *in principle* supported by Verilog, but not by all synthesis tools

⇒ We are only using edge-triggered flip-flops

- Declaration of variable that can be used as a 1-bit memory:


```
reg q;
```

- `always` block for assignment of `reg` variables.
Execution depends on variables in *sensitivity list*.

```
always @(sensitivity list)
begin
    ...
end
```

- Edge detection `posedge a` and `negedge a`
- (Non-blocking) assignment `<=`
- Common structuring elements within an `always` block: `if`, `case`


Example 1: D-Flip-Flop with enable input

 

```
module dfpe(  
    input clk,  
    input din,  
    input enable,  
    output out  
);
```

```
endmodule
```


Example 1: D-Flip-Flop with enable input

 

```
module dfpe(  
    input clk,  
    input din,  
    input enable,  
    output out  
);  
    reg q;
```

```
endmodule
```

Example 1: D-Flip-Flop with enable input

 

```


module dffe(
    input clk,
    input din,
    input enable,
    output out
);
    reg q;
    always @(posedge clk)
    begin

        end

    endmodule

```

Example 1: D-Flip-Flop with enable input

 


```

module dfpe(
    input clk,
    input din,
    input enable,
    output out
);
    reg q;
    always @(posedge clk)
    begin
        if (enable)
            q <= din;
    end

endmodule

```

Example 1: D-Flip-Flop with enable input

 

```

module dfpe(
    input clk,
    input din,
    input enable,
    output out
);
    reg q;
    always @(posedge clk)
    begin
        if (enable)
            q <= din;
    end
    assign out = q;
endmodule

```

Example II: Cyclic 4-bit counter

```
module counter (  
    input clock,  
    input reset,  
    output [3:0] count  
);  
    reg [3:0] q;  
    always @(posedge clock)  
    begin  
        if (reset)  
            q <= 4'b0;  
        else  
            q <= q + 1'b1;  
        end  
    assign count = q;  
endmodule
```


Example II: Cyclic n -bit counter

```
module counter #(parameter N = 4) (  
    input clock,  
    input reset,  
    output [N-1:0] count  
);  
    reg [N-1:0] q;  
    always @(posedge clock)  
    begin  
        if (reset)  
            q <= 'b0;  
        else  
            q <= q + 1'b1;  
        end  
        assign count = q;  
    endmodule
```

Outlook: always for combinatorial circuits

```
wire x, y;  
assign x = a ? b : c;  
assign y = a ? b : d ? c : e;
```

```
wire x, y;  
assign x = a ? b : c;  
assign y = a ? b : d ? c : e;
```

```
reg x, y;  
always @*  
begin  
    if (a) begin  
        x = b;  
        y = b;  
    end else begin  
        x = c;  
        if (d)  
            y = c;  
        else  
            y = e;  
        end  
    end  
end
```

⇒ reg and always can also be used for combinatorial circuits

Blocking assignment

```
reg x, y;  
always @(posedge clk)  
begin  
    x = y;  
    y = x;  
end
```

Assignments are blocking,
i.e., they are executed **sequentially**
⇒ x and y are equal

Non-blocking assignment

```
reg x, y;  
always @(posedge clk)  
begin  
    x <= y;  
    y <= x;  
end
```

Assignments are non-blocking, i.e.,
are conceptually executed in parallel
⇒ x and y are exchanged

- 1 For memory elements use always `@(pos/negedge clk),`
non-blocking assignments `<=` and `reg`
- 2 For simple combinatorial circuits `assign,`
blocking assignments `=` and `wire`
- 3 For complex combinatorial circuits always `@*,`
blocking assignments `=` and `reg`
- 4 Never assign a signal multiple times (`wire` or `reg`),
i.e., no two *active* assignments at the same time

- 1 For memory elements use `always @ (pos/negedge clk),`
non-blocking assignments `<=` and `reg`
- 2 For simple combinatorial circuits `assign,`
blocking assignments `=` and `wire`
- 3 For complex combinatorial circuits `always @*,`
blocking assignments `=` and `reg`
- 4 Never assign a signal multiple times (`wire` or `reg`),
i.e., no two *active* assignments at the same time

Follow these rules

⇒ Otherwise: *strange* often, subtle errors

1 Introduction

2 Verilog for Hardware Synthesis

- Combinatorial circuits
- Sequential circuits

3 Simulation

- Test benches

4 *Optional:* FPGA and Synthesis

A **test bench** is a Verilog module that

- 1 instantiates a module-under-test M ,
- 2 generates input stimuli for M , and
- 3 *optionally* tests the correctness of the outputs of M automatically.

Use of *delays*:

```
statement 1; #5; statement 2; delays the sequential execution
```

Use of *delays*:

statement 1; #5; statement 2; **delays the sequential execution**

■ Once

```
initial
begin
    reset <= 1;
    #22;
    reset <= 0;
end
```

Use of *delays*:

statement 1; #5; statement 2; **delays the sequential execution**

■ Once

```
initial
begin
    reset <= 1;
    #22;
    reset <= 0;
end
```

■ Periodically

```
always
begin
    clk <= 1; #5; clk <= 0; #5;
end
```

Use of *delays*:

statement 1; #5; statement 2; **delays the sequential execution**

■ Once

```
initial
begin
    reset <= 1;
    #22;
    reset <= 0;
end
```

■ Periodically

```
always
begin
    clk <= 1; #5; clk <= 0; #5;
end
```

■ Multiple times with repeat (x)

Additional functions to control the simulation, **non-synthesizable**, thus mainly used in test benches

- `$display` output similar to `printf` in C
- `$finish` stops the simulation
- `$readmemb/$readmemh` initializes memory elements
- `$dumpfile/$dumpvars` outputs variables as waveforms

Icarus: open-source simulator for Verilog

<http://iverilog.icarus.com/>

GTKWave: open-source visualization and analysis tool for waveforms

<http://gtkwave.sourceforge.net/>

Icarus: open-source simulator for Verilog

<http://iverilog.icarus.com/>

GTKWave: open-source visualization and analysis tool for waveforms

<http://gtkwave.sourceforge.net/>

Demo

1 Introduction

2 Verilog for Hardware Synthesis


- Combinatorial circuits
- Sequential circuits

3 Simulation

- Test benches


4 *Optional:* FPGA and Synthesis

■ Look-up table (4LUT)

 


Can be used to implement an arbitrary Boolean function from $\mathbb{B}^4 \rightarrow \mathbb{B}$.

■ Register

 

 
Structure of a Field Programmable Gate Array¹




In addition: Dedicated components:
Memory blocks (8192 Bits), multipliers (9 Bits), etc.

¹http://commons.wikimedia.org/wiki/File:Fpga_structure.svg

Structure of an FPGA — Network

 

Structure of an FPGA — Network

 

- 1 Analysis and elaboration
 - ▶ Syntax and semantics
 - ▶ Find dedicated components
- 2 Synthesis
 - ▶ Translation into logical blocks
- 3 Fitter
 - ▶ Place-and-Route
- 4 Assembler
- 5 Timing analysis
 - ▶ Computation of critical paths and maximal frequency

Example: Pong



[https://commons.wikimedia.org/wiki/File:APF_TV_Fun_\(with_paddle_model\).jpg](https://commons.wikimedia.org/wiki/File:APF_TV_Fun_(with_paddle_model).jpg)

Original from: <http://www.flickr.com/photos/adampsyche/3085132136/>

Brainstorming: Pong game logic

State?

Behavior?

Brainstorming: Pong game logic

State?

- Position of left paddle
- Position of right paddle
- Position/speed of ball

Behavior?

State?

- Position of left paddle
- Position of right paddle
- Position/speed of ball

Behavior?

- Collision paddles
- Collision borders

Brainstorming: Pong game logic

State?

- Position of left paddle
- Position of right paddle
- Position/speed of ball

Behavior?

- Collision paddles
- Collision borders

Verilog implementation:

<https://github.com/ttudziak/fpga-pong>

- Retro games <http://bit.ly/1r9EMks>
- Signal processing
- Hardware Prototyping
- Encryption of network traffic <http://bit.ly/WkzpcE>
- Parallel algorithms <http://bit.ly/ZYOTJG>,
DES attack (2003) <http://bit.ly/11ZKxze>
- Earlier: Bitcoin mining (now: ASICs)