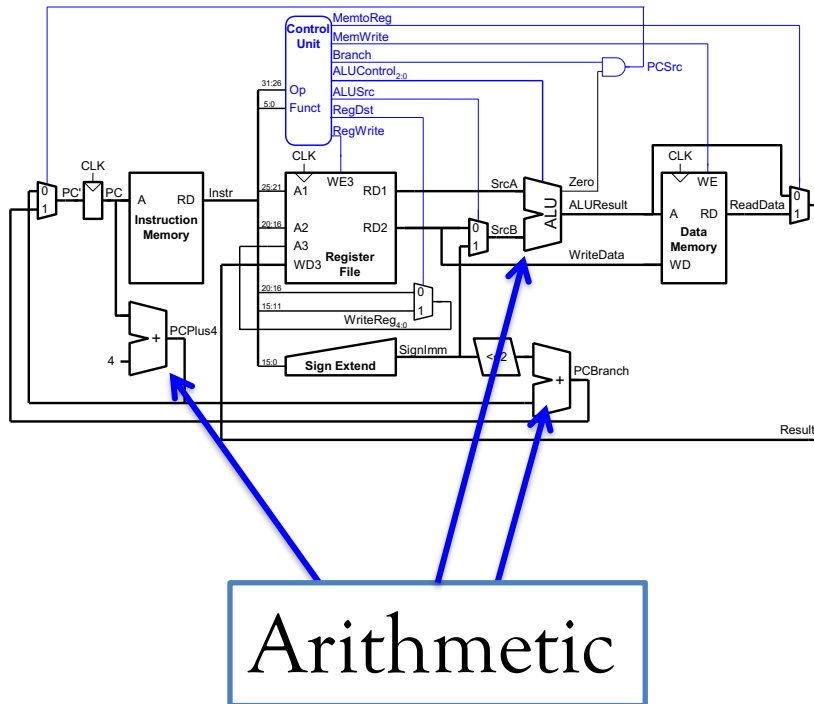


Arithmetic Circuits: Adders

Becker/Molitor, Chapter 9.2

Jan Reineke
Universität des Saarlandes

Roadmap: Computer architecture



1. Combinatorial circuits: Boolean Algebra/Functions/Expressions/Synthesis
2. Number representations
3. **Arithmetic Circuits:**
Addition, Multiplication, Division, ALU
4. Sequential circuits: Flip-Flops, Registers, SRAM, Moore and Mealy automata
5. Verilog
6. Instruction Set Architecture
7. Data path & Control path
8. Performance: RISC vs. CISC, Pipelining, Memory Hierarchy

Representation of **natural numbers**


Let $a = a_{n-1} \dots a_1 a_0$ be a sequence of numerals from the positional numeral system $(b, Z, \delta) = (2, \{0, 1\}, id)$.

(We call such numbers *binary numbers*.)

Then the value $\langle a \rangle$ of a is:

$$\langle a \rangle = \langle a_{n-1} \dots a_1 a_0 \rangle = \sum_{i=0}^{n-1} b^i \cdot \delta(a_i)$$

Adders

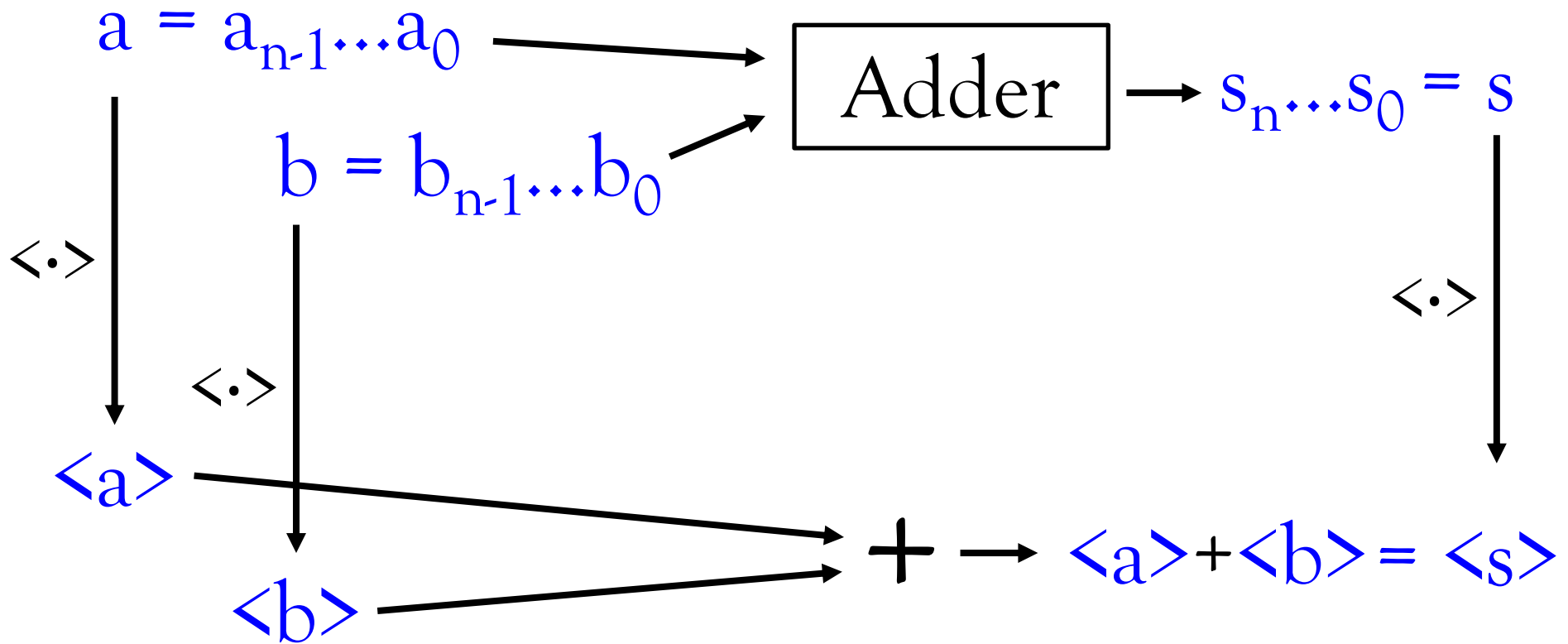

Adder (with carry-in)

Given: 2 positive binary numbers

$$\langle a \rangle = \langle a_{n-1} \dots a_0 \rangle,$$

$$\langle b \rangle = \langle b_{n-1} \dots b_0 \rangle,$$

and a carry-in $c \in \{0,1\}$.

Wanted: Circuit computing the binary representation of

$$\langle s \rangle = \langle a \rangle + \langle b \rangle + c.$$

How many bits do we need to represent s ?

Because $\langle a \rangle + \langle b \rangle + c \leq 2 \cdot (2^n - 1) + 1 = 2^{n+1} - 1$

$n+1$ bits suffice for s ,

i.e., a circuit with $n+1$ outputs.

Definition: Adder

Definition (Adder):


An **n-bit adder** is a circuit that computes the following Boolean function:

$$+_n : \mathbf{B}^{2n+1} \rightarrow \mathbf{B}^{n+1},$$

$$(a_{n-1}, \dots, a_0, b_{n-1}, \dots, b_0, c) \rightarrow (s_n, \dots, s_0) \quad \text{with}$$

$$\langle s \rangle = \langle s_n \dots s_0 \rangle = \langle a_{n-1} \dots a_0 \rangle + \langle b_{n-1} \dots b_0 \rangle + c$$

Schematic of an n-bit adder

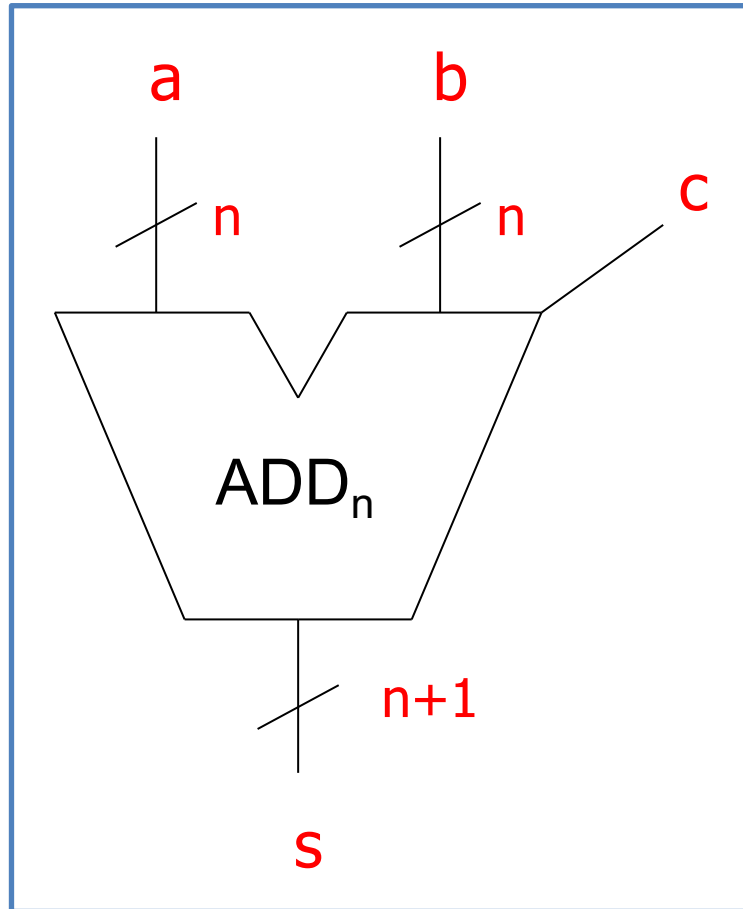

Back to the basics: Grade school addition

Adding as you learned it
in grade school:

$$\begin{array}{r} 1011 \\ + 0110 \\ + \text{red scribbles} 0 \\ \hline \text{red scribbles} \end{array}$$

carry-in

Half adder (HA)

Half adders may be used to sum up two 1-Bit numbers *without* carry-in:
It computes the following function:

$$ha : \mathbf{B}^2 \rightarrow \mathbf{B}^2$$

$$\text{with } ha(a_0, b_0) = (s_1, s_0)$$

$$\begin{aligned} \text{with } \langle s_1 s_0 \rangle &= 2s_1 + s_0 \\ &= a_0 + b_0 = \langle a_0 \rangle + \langle b_0 \rangle \end{aligned}$$


Truth table of the *HA*

a_0	b_0	ha_1	ha_0
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Thus:

$$ha_0 = a_0 \oplus b_0 \quad ha_1 = a_0 \wedge b_0$$

Half adder circuit

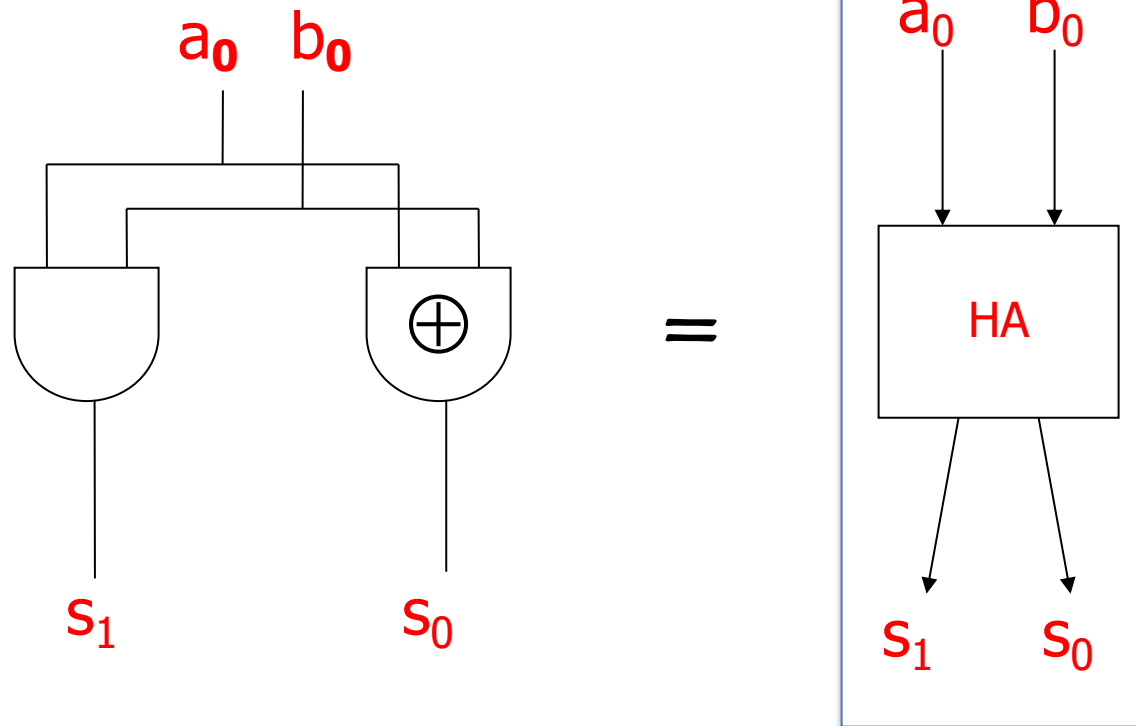

Cost and depth of a half adder:

$$C(HA) = 2, \text{ depth}(HA) = 1$$

Full adder (FA)

a_0	b_0	c	fa_1	fa_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

From the table we can derive:

$$fa_0 = a_0 \oplus b_0 \oplus c = ha_0(c, ha_0(a_0, b_0))$$

$$\begin{aligned} fa_1 &= a_0 \wedge b_0 \vee c \wedge (a_0 \oplus b_0) \\ &= ha_1(a_0, b_0) \vee ha_1(c, ha_0(a_0, b_0)) \end{aligned}$$

Full adder composed from HAs



From the table we can derive:

$$fa_0 = a_0 \oplus b_0 \oplus c = ha_0(c, ha_0(a_0, b_0))$$

$$\begin{aligned} fa_1 &= a_0 \wedge b_0 \vee c \wedge (a_0 \oplus b_0) \\ &= ha_1(a_0, b_0) \vee ha_1(c, ha_0(a_0, b_0)) \end{aligned}$$


Cost and depth of a FA :

$$C(FA) = 5, \text{depth}(FA) = 3$$

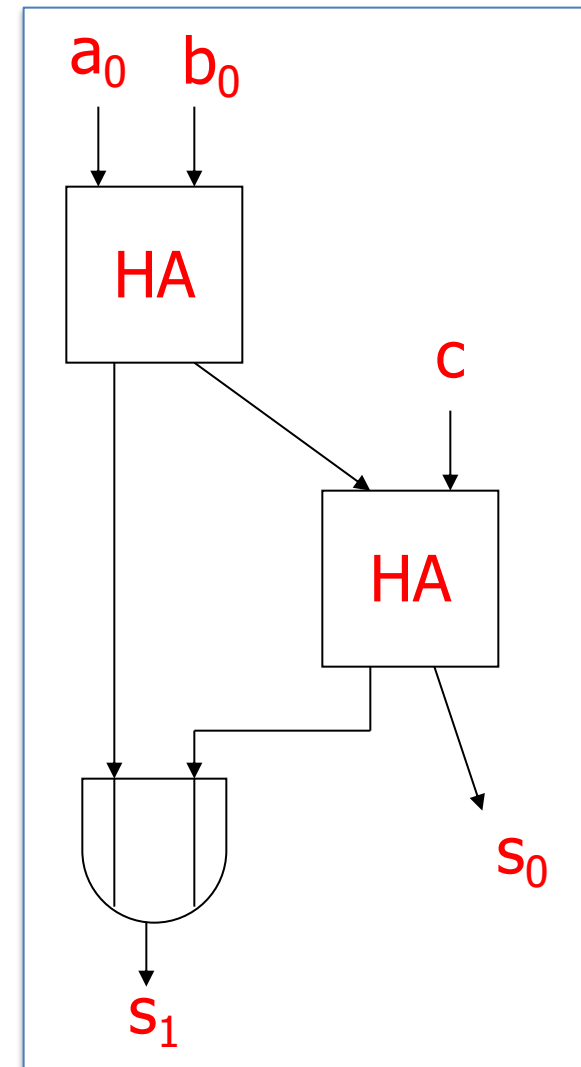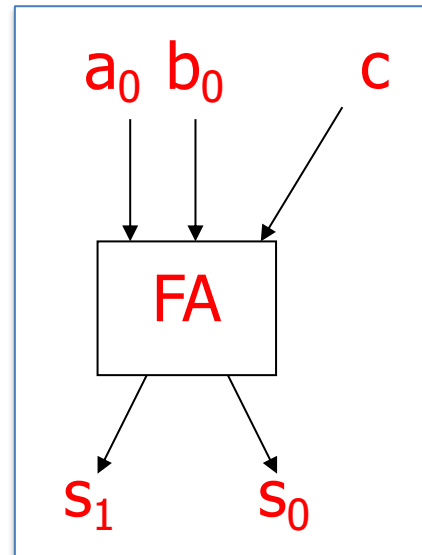

Implementing the “school method”: Ripple-carry adder (RC)

(also called Carry-chain adder)

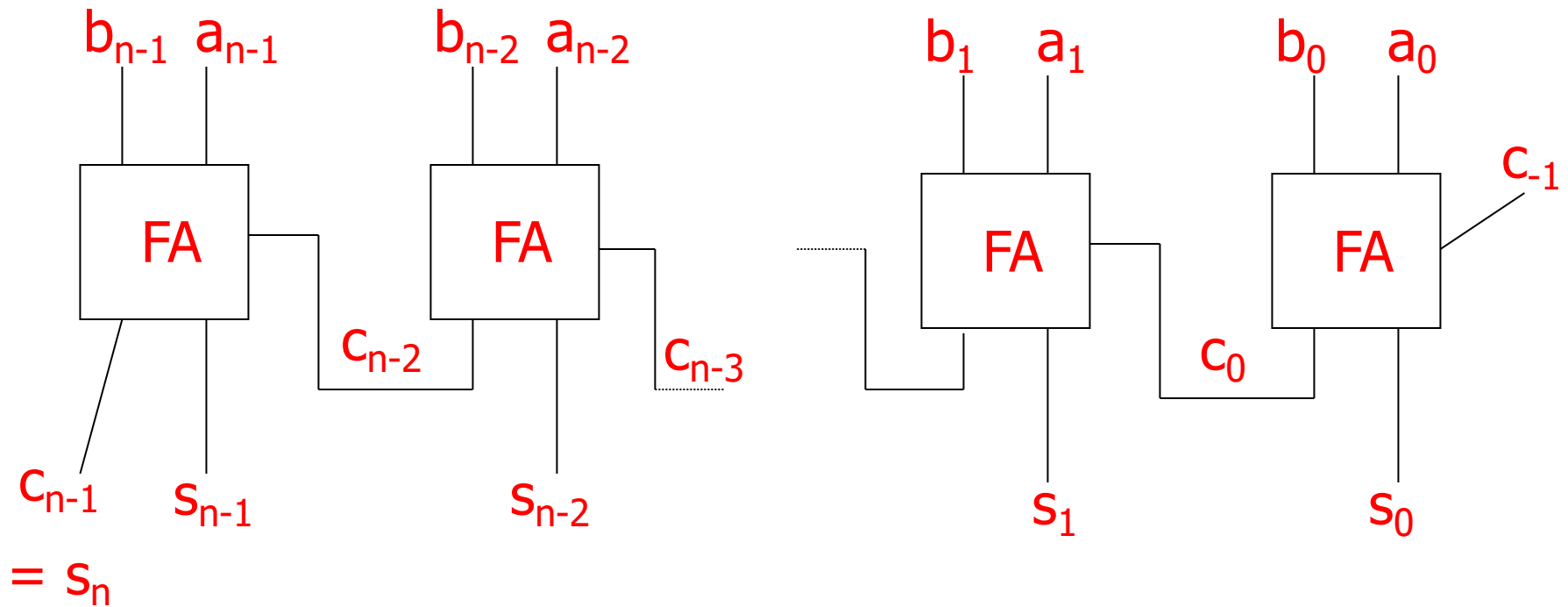

Implementing the “school method”: Ripple-carry adder (RC)

Hierarchical construction:
(inductive definition)


For $n=1$: $RC_1 = FA$

For $n>1$: Circuit RC_n is defined as follows

Notation:

We refer to the carry-in with c_1 , and the carry from position i to $i+1$ with c_i .

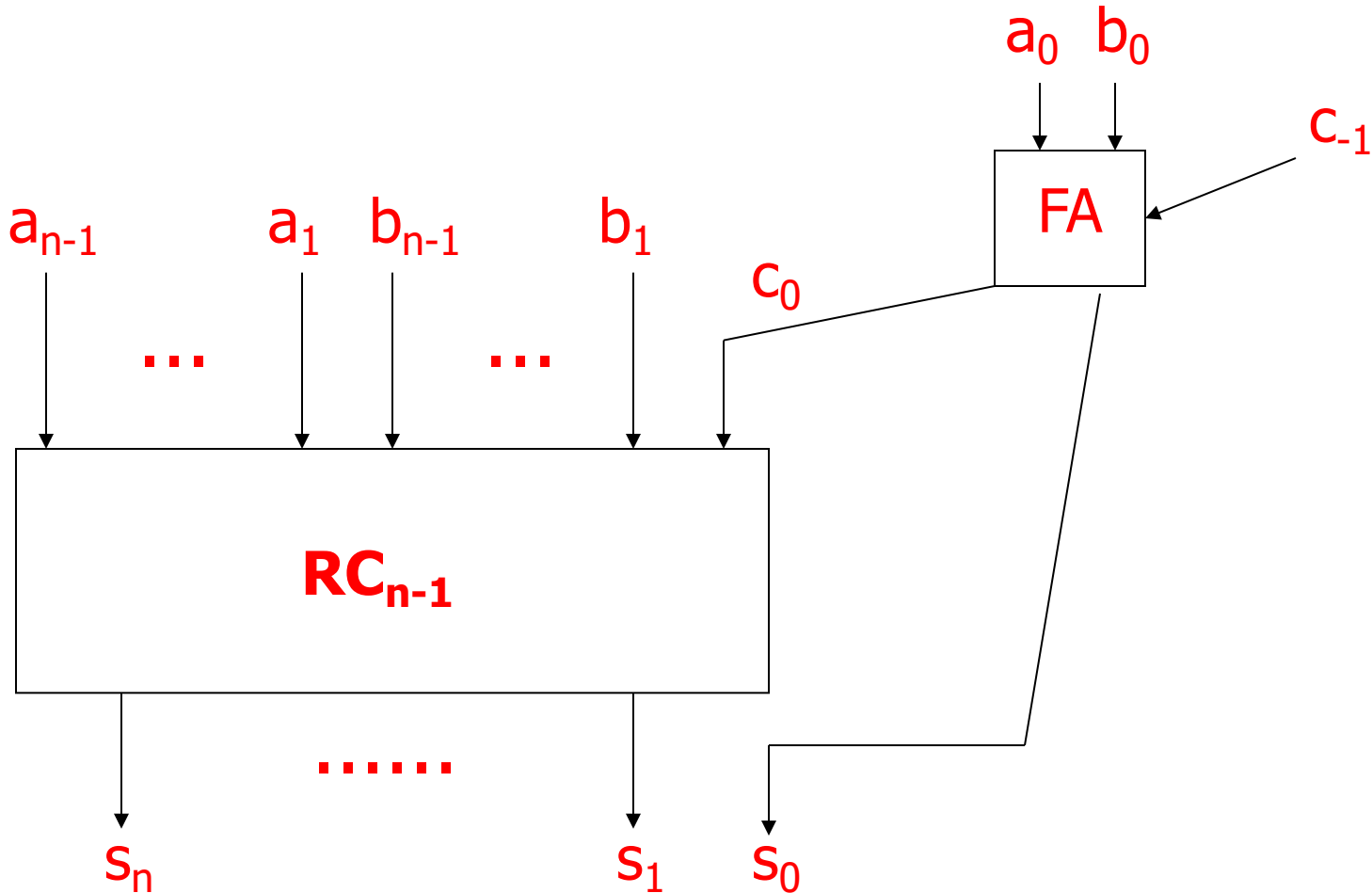Recursive construction of an n-bit Ripple-carry adder (RC_n)



Correctness of the RC_n

Theorem: The RC_n circuit is an n-bit adder.

I.e., it computes the function

$$+_n : \mathbf{B}^{2n+1} \rightarrow \mathbf{B}^{n+1},$$

$$(a_{n-1}, \dots, a_0, b_{n-1}, \dots, b_0, c) \rightarrow (s_n, \dots, s_0) \quad \text{with}$$

$$\langle s \rangle = \langle s_n \dots s_0 \rangle = \langle a_{n-1} \dots a_0 \rangle + \langle b_{n-1} \dots b_0 \rangle + c$$

Correctness of the RC_n : Proof

Proof by induction:

- $n=1$: ✓

- $n-1 \rightarrow n$:

Input to RC_n : $(a_{n-1}, \dots, a_0, b_{n-1}, \dots, b_0, c_{-1})$

Show that the output (s_n, \dots, s_0) of RC_n satisfies

$$\langle s \rangle = \langle s_n \dots s_0 \rangle = \langle a_{n-1} \dots a_0 \rangle + \langle b_{n-1} \dots b_0 \rangle + c_{-1}$$

We know that: $\langle c_0, s_0 \rangle = a_0 + b_0 + c_{-1}$ (FA)

And by inductive hypothesis:

$$\text{For } RC_{n-1}: \langle s_n \dots s_1 \rangle = \langle a_{n-1} \dots a_1 \rangle + \langle b_{n-1} \dots b_1 \rangle + c_0$$

Putting it all together:


$$\langle s_n \dots s_0 \rangle = 2 \cdot \langle s_n \dots s_1 \rangle + s_0$$

$$\text{(I.H.)} \quad = 2 \cdot (\langle a_{n-1} \dots a_1 \rangle + \langle b_{n-1} \dots b_1 \rangle + c_0) + s_0$$

$$\text{(FA)} \quad = 2 \cdot \langle a_{n-1} \dots a_1 \rangle + a_0 + 2 \cdot \langle b_{n-1} \dots b_1 \rangle + b_0 + c_{-1}$$

$$= \langle a \rangle + \langle b \rangle + c_{-1}$$

Cost and depth of Ripple-carry adders

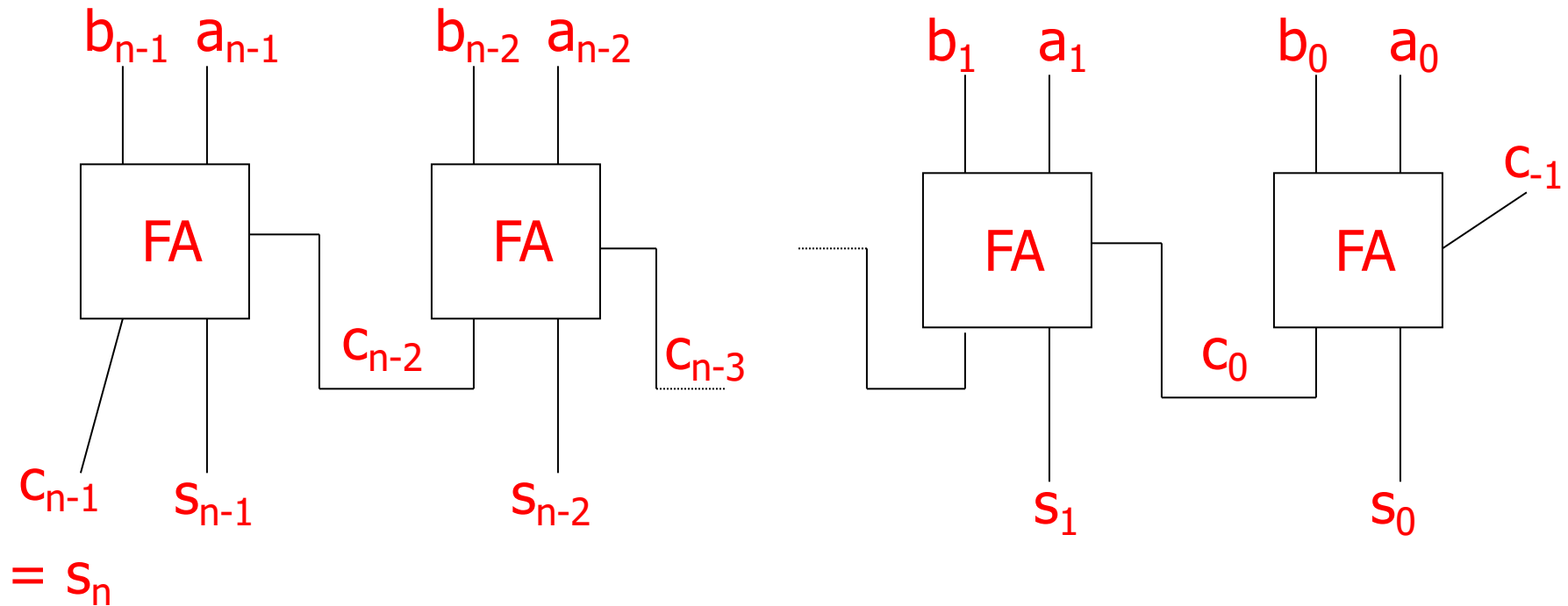


Cost of RC_n ?

$$C(RC_n) = n \cdot C(FA) = 5n$$

Depth of RC_n ?

$$\text{depth}(RC_n) = 3 + 2(n-1) \overset{!}{<} 3n \text{ (for } n > 1\text{)}$$

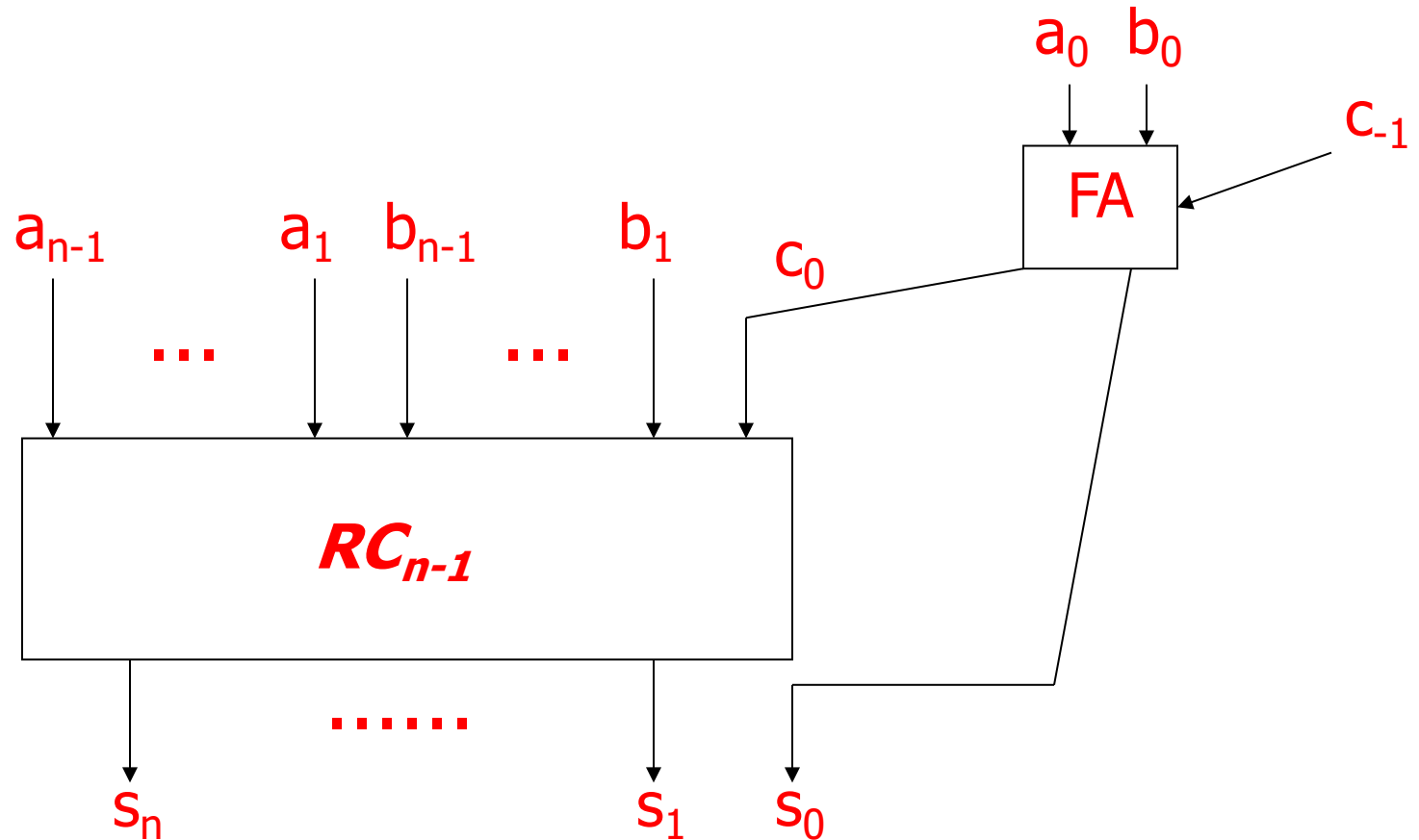Cost and depth of Ripple-carry adders (recursive)



Cost of RC_n : $C(RC_n) = C(FA) + C(RC_{n-1}) = 5 + C(RC_{n-1})$

Depth of RC_n : $\text{depth}(RC_n) = 3 + \text{depth}(RC_{n-1}) - 1 = 3 + 2(n-1)$

Some more important circuits

- n-bit incrementer
- n-bit multiplexer

Definition: n-bit incrementer

An **n-bit incrementer** computes the following function:

$$inc_n : \mathbf{B}^{n+1} \rightarrow \mathbf{B}^{n+1},$$

$$(a_{n-1}, \dots, a_0, c) \rightarrow (s_n, \dots, s_0) \quad \text{with}$$

$$\langle s_n \dots s_0 \rangle = \langle a \rangle + c$$

Incrementer

An Incrementer is an adder with $b_i=0$ for all i .

→ Replaces the FAs in RC_n by HAs .

Cost and depth:

$$C(INC_n) = n \cdot C(HA) = 2n$$

$$\text{depth}(INC_n) = n \cdot \text{depth}(HA) = n$$


Definition: n-bit multiplexer

An **n-bit multiplexer** (MUX_n) is a circuit that computes the following function:

$$\text{sel}_n : \mathbf{B}^{2n+1} \rightarrow \mathbf{B}^n \quad \text{with}$$


$$\begin{aligned} \text{sel}_n(a_{n-1}, \dots, b_{n-1}, \dots, b_0, s) \\ = \begin{cases} (a_{n-1}, \dots, a_0) : \text{if } s = 1 \\ (b_{n-1}, \dots, b_0) : \text{if } s = 0 \end{cases} \end{aligned}$$
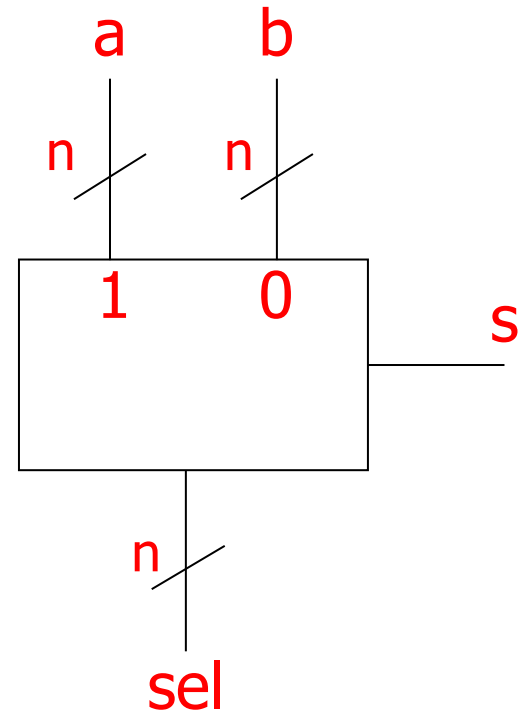
$$(\text{sel}_n)_i = s \cdot a_i + \bar{s} \cdot b_i$$



Schematic of an n-bit multiplexer

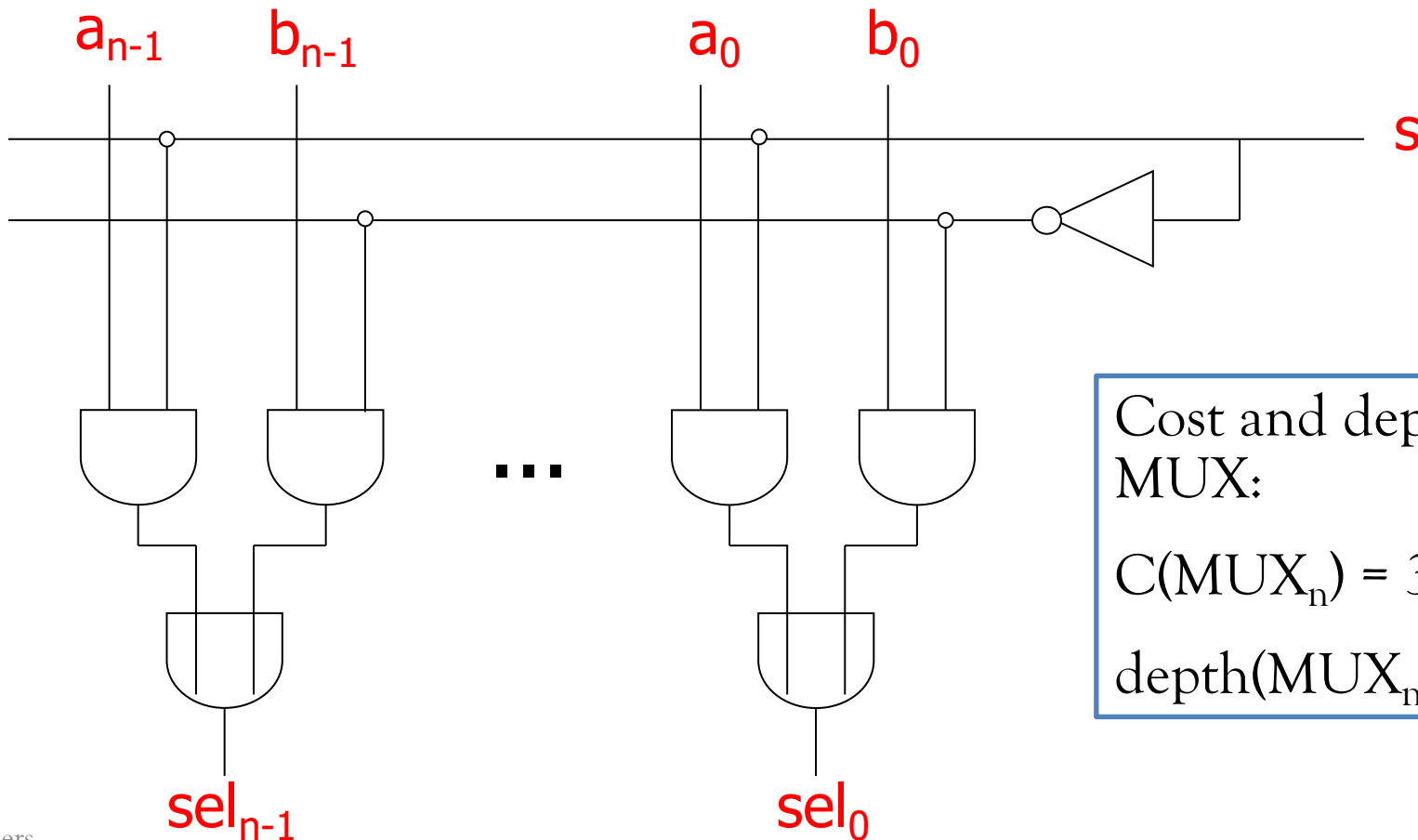Based on the equation: $(sel_n)_i = s \cdot a_i + \bar{s} \cdot b_i$



Cost and depth of a MUX:


$$C(\text{MUX}_n) = 3n + 1$$

$$\text{depth}(\text{MUX}_n) = 3$$

Back to adders

Brainstorming:

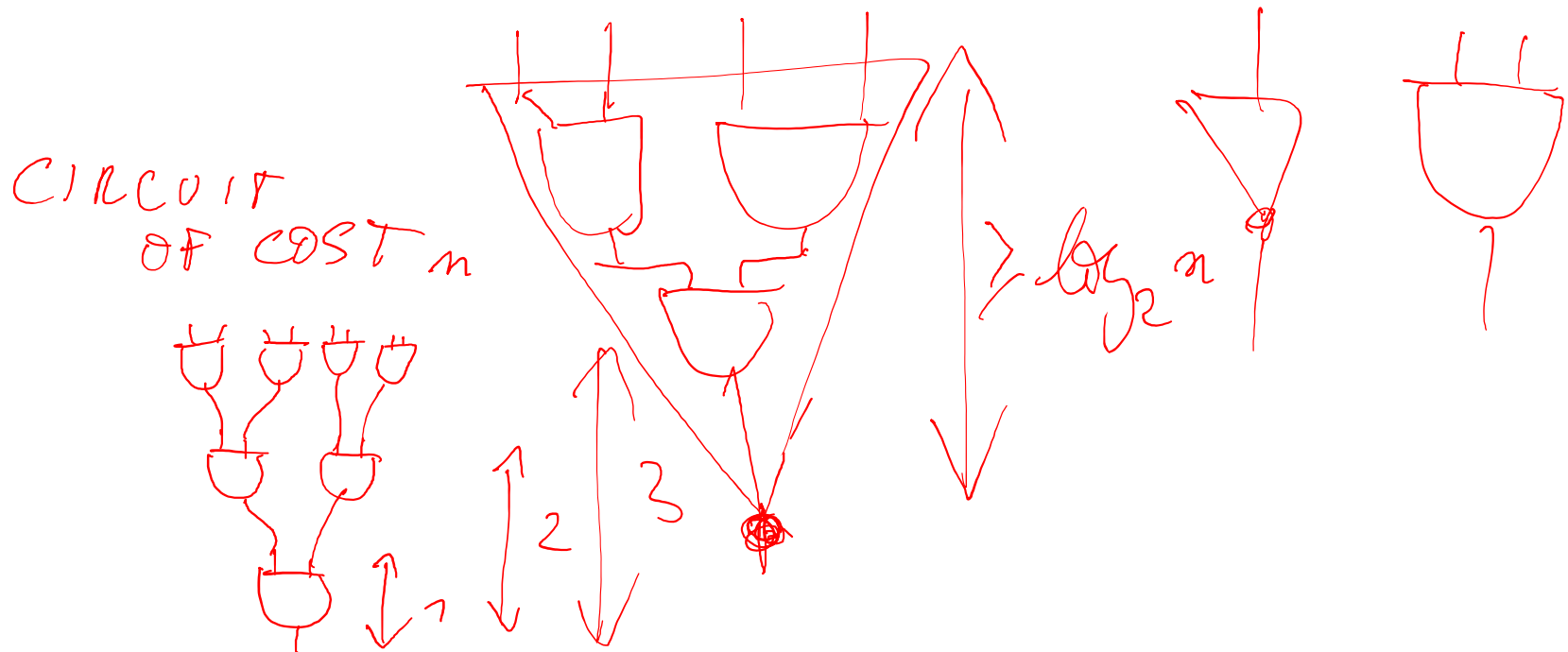- Are there cheaper and faster adders than RC_n ?
- Can we construct a constant-depth adder, independently of n ?



Back to adders

Brainstorming:

- Are there cheaper and faster adders than RC_n ?
- Can we construct a constant-depth adder, independently of n ?

Lower bounds!

$$C(+_n) \geq 2n, \text{ depth}(+_n) \geq \log(n) + 1$$

Observation: Output s_n depends on all $2n+1$ inputs!


We use gates with at most 2 inputs.

Binary trees with $2n+1$ leaves have $2n$ inner nodes.

Binary trees with n leaves have depth $\geq \lceil \log n \rceil$.


In the following, let $n = 2^k$.

Brainstorming: Faster adders

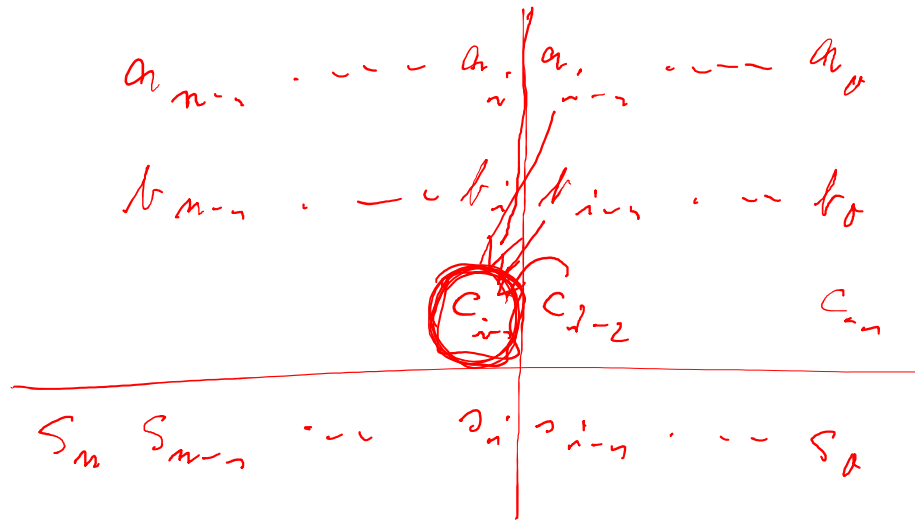

Idea: „Divide and Conquer“:

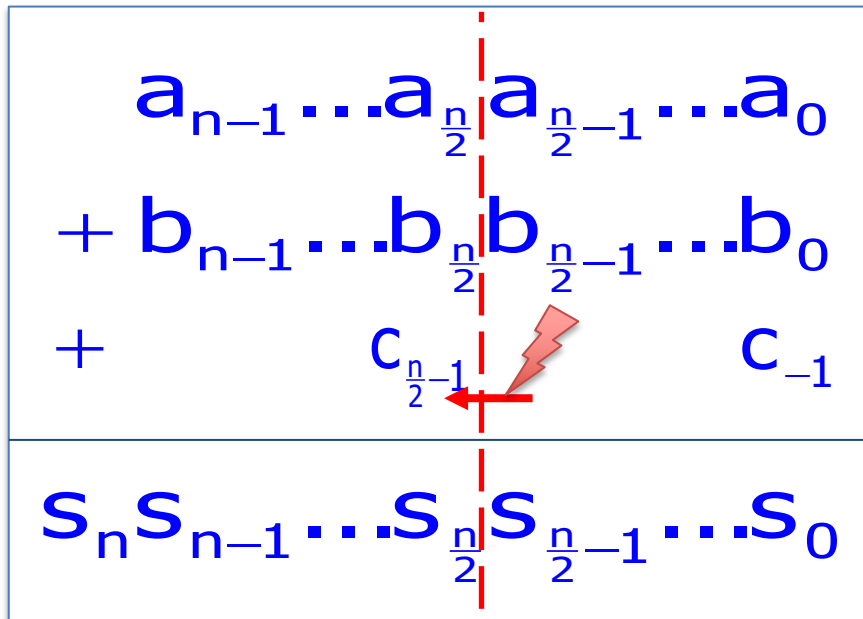Employ **parallel processing** to reduce the depth!



More *precisely*:

Compute **upper** and **lower** half of result in **parallel**.


Problem:

Dependency of the upper half of the result **on carry** from lower half.

Solution:

Computer upper half **for both possible values** of the carry and pick the correct one later.

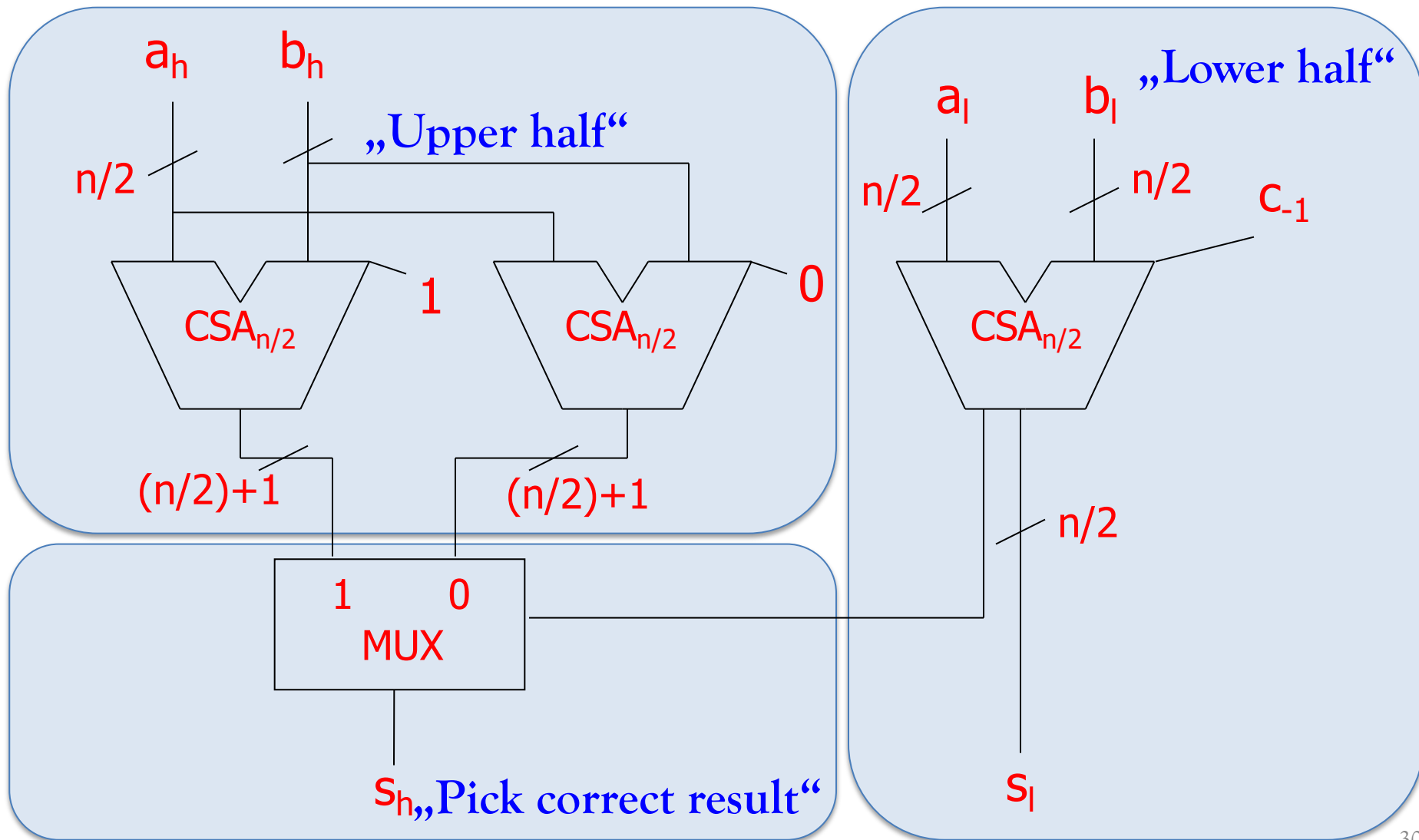Schematic of a conditional-sum adder (CSA_n)



On the complexity of the CSA_n

- We have: $\text{CSA}_1 = \text{FA}$.
- A CSA_n consists of 3 $\text{CSA}_{n/2}$.

Brainstorming: Depth of the CSA_n

How does $\text{depth}(\text{CSA}_n)$ evolve depending on n ?

$$\begin{aligned}\text{depth}(\text{CSA}_n) &= \text{depth}(\text{CSA}_{n/2}) + \text{depth}(\text{MUX}_{(n/2)+1}) \\ &= \text{depth}(\text{CSA}_{n/2}) + 3 \\ &= \text{depth}(\text{CSA}_{n/4}) + 3 + 3 \\ &= \text{depth}(\text{CSA}_{n/8}) + 3 + 3 + 3 \\ &= \text{depth}(\text{CSA}_{n/2^k}) + 3k \\ &= \text{depth}(\text{CSA}_1) + 3k && (n = 2^k, k = \log_2 n) \\ &= \text{depth}(\text{FA}) + 3k \\ &= 3(k+1) \\ &= 3 \log_2 n + 3\end{aligned}$$

Depth of the CSA_n

Theorem (Depth of the CSA_n):

$$\text{depth}(\text{CSA}_n) = 3 \log_2 n + 3$$

Proof:

By induction over n .

- Induction base ($n=1$):

$$\text{depth}(\text{CSA}_1) = \text{depth}(\text{FA}) = 3.$$

- Induction step ($n>1$):

$$\begin{aligned} \text{depth}(\text{CSA}_n) &= \text{depth}(\text{CSA}_{n/2}) + \text{depth}(\text{MUX}_{(n/2)+1}) \\ &= 3 \log_2 (n/2) + 3 + \text{depth}(\text{MUX}_{(n/2)+1}) \quad (\text{inductive hypothesis}) \\ &= 3 \log_2 (n/2) + 3 + 3 \quad (\text{depth of the multiplexer}) \\ &= 3 ((\log_2 n) - (\log_2 2)) + 3 + 3 \\ &= 3 ((\log_2 n) - 1) + 3 + 3 \\ &= 3 \log_2 n + 3 \end{aligned}$$

Reminder:

We assume that n is a power of two.

Remember:

$$\log(a/b) = (\log a) - (\log b)$$

Lower bound on the cost of the CSA_n

How does the cost $C(\text{CSA}_n)$ evolve depending on n ?

$$C(\text{CSA}_1) = C(\text{FA}) = 5$$

$$C(\text{CSA}_n) = 3 \cdot C(\text{CSA}_{n/2}) + C(\text{MUX}_{(n/2)+1})$$

$$= 3 \cdot C(\text{CSA}_{n/2}) + 3 \cdot n/2 + 4$$

(*) To derive a lower bound we ignore the multiplexer.

$$\stackrel{(*)}{\geq} 3 \cdot C(\text{CSA}_{n/2})$$

$$\geq 3 \cdot 3 \cdot C(\text{CSA}_{n/4})$$

$$\geq 3^k \cdot C(\text{CSA}_{n/2^k})$$

$$= 3^k \cdot C(\text{CSA}_1)$$

$$= 5 \cdot 3^{\log n}$$

Reminder:
 $C(\text{MUX}_n) = 3n + 1$

$$(k = \log_2 n)$$

Lower bound on the cost of the CSA_n

Theorem (Cost of the CSA_n):

$$C(\text{CSA}_n) \geq 5 \cdot 3^{\log n}$$

Proof (by induction over n):

Induction base ($n = 1$):

$$C(\text{CSA}_1) = C(\text{FA}) = 5 \geq 5 = 5 \cdot 3^{\log 1}$$

Induction step ($n > 1$):

$$\begin{aligned} C(\text{CSA}_n) &= 3 \cdot C(\text{CSA}_{n/2}) + C(\text{MUX}_{(n/2)+1}) \\ &\geq 3 \cdot C(\text{CSA}_{n/2}) \\ &\geq 3 \cdot 5 \cdot 3^{\log(n/2)} && \text{(inductive hypothesis)} \\ &= 5 \cdot 3 \cdot 3^{(\log n)-1} \\ &= 5 \cdot 3^{\log n} \end{aligned}$$

Lower bound on the cost of the CSA_n

What is $3^{\log n}$?

$$3^{\log n} = (2^{\log 3})^{\log n} = 2^{\log 3 \cdot \log n} = (2^{\log n})^{\log 3} = n^{\log 3}$$

$$n^{\log 3} \approx n^{1.58}$$

For example:

$$64^{\log 3} = 3^{\log 64} = 3^6 = 729$$

Exact cost of the CSA_n

Taking into account the cost of the multiplexer, the exact cost of the CSA_n is:

$$C(\text{CSA}_n) = 10n^{\log 3} - 3n - 2$$

Thus, the conditional-sum adder is
very fast, but also **pretty expensive**!

Questions: Are there adders with

- **linear cost** (like the ripple-carry adder), and
- **logarithmic depth** (like the conditional-sum adder)?

Excursion:

Addition of numbers in two's complement

Can we use **n-bit adders** for numbers in two's complement?

Observation:

$$[d_{n-1} \dots d_0]_2 = \langle d_{n-2} \dots d_0 \rangle - d_{n-1} \cdot 2^{n-1} \text{ and } \langle d_{n-1} \dots d_0 \rangle = \langle d_{n-2} \dots d_0 \rangle + d_{n-1} \cdot 2^{n-1}$$

$$\text{So } \langle d_{n-1} \dots d_0 \rangle - [d_{n-1} \dots d_0]_2 = d_{n-1}(2^{n-1} + 2^{n-1}) = d_{n-1}2^n.$$

$$\text{I.e. } \langle d_{n-1} \dots d_0 \rangle \equiv [d_{n-1} \dots d_0]_2 \pmod{2^n}.$$

Excursion:

Addition of numbers in two's complement

Theorem:

Let $a, b \in \mathbf{B}^n$, $c_{n-1}, c_{-1} \in \mathbf{B}$ and $s \in \mathbf{B}^n$,
such that $\langle c_{n-1}, s \rangle = \langle a \rangle + \langle b \rangle + c_{-1}$.

Then: $[s]_2 \equiv [a]_2 + [b]_2 + c_{-1} \pmod{2^n}$.

Proof:

1. $[a]_2 \equiv \langle a \rangle \pmod{2^n}$, $[b]_2 \equiv \langle b \rangle \pmod{2^n}$, $[s]_2 \equiv \langle s \rangle \pmod{2^n}$
2. $\langle a \rangle + \langle b \rangle + c_{-1} = \langle c_{n-1}, s \rangle \equiv \langle s \rangle \pmod{2^n}$
3. $[a]_2 + [b]_2 + c_{-1} \overset{(1.)}{\equiv} \langle a \rangle + \langle b \rangle + c_{-1} \overset{(2.)}{\equiv} \langle c_{n-1}, s \rangle \overset{(1.)}{\equiv} \langle s \rangle \equiv [s]_2 \pmod{2^n}$

Excursion:

Addition of numbers in two's complement

Observation:

The range of numbers covered by n-bit two's complement is $R_n = \{-2^{n-1}, \dots, 2^{n-1}-1\}$

→ There are **no two** different values in R_n that are equal modulo 2^n .


Thus:

If the result of the addition is representable in n-bit two's complement, then it is computed correctly by an n-bit adder.

Excursion:


Addition of numbers in two's complement

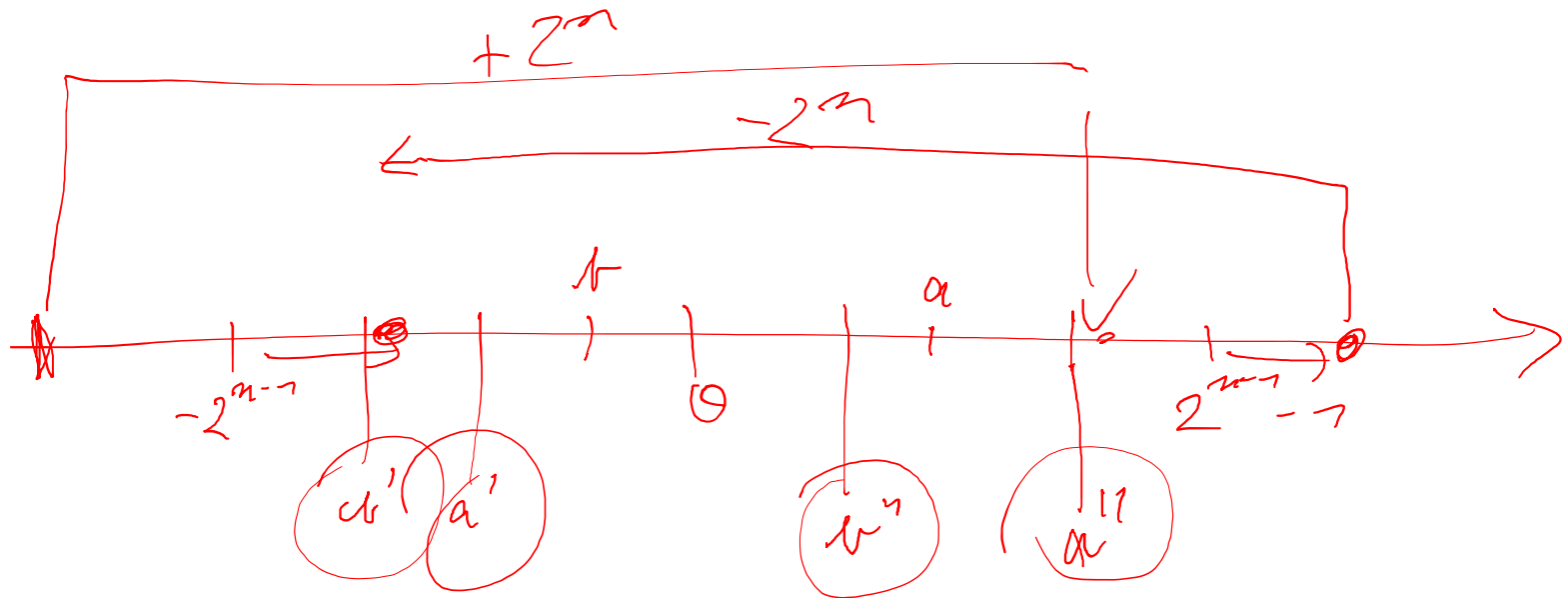Question: When is the result of the addition of two n -bit two's complement numbers not representable in n -bit two's complement?



Discovering an overflow of an n-bit adder

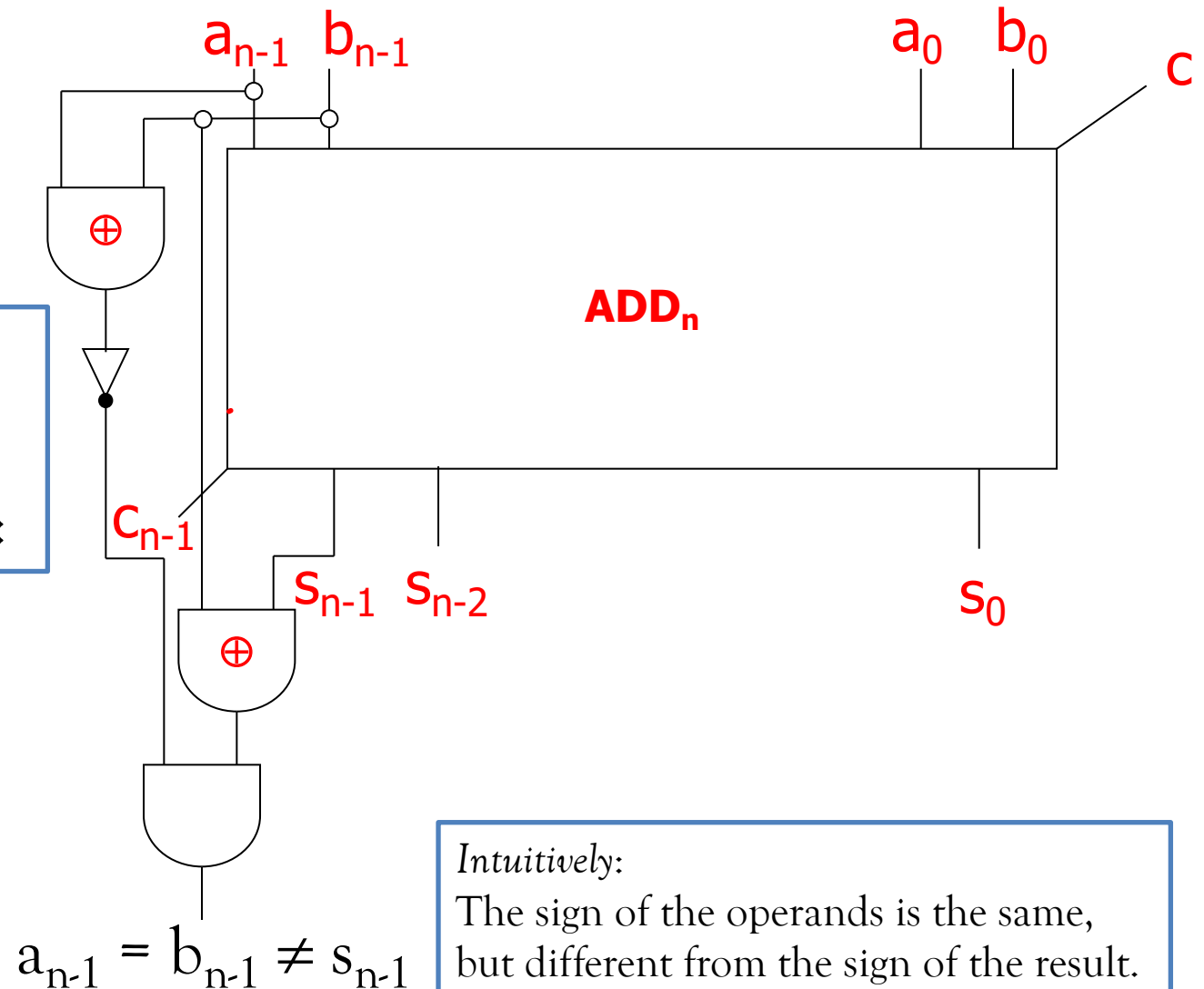Circuit detects whether an overflow occurs:



Intuitively:

The sign of the operands is the same, but different from the sign of the result.

Excursion:

Addition of numbers in two's complement

Theorem:

Let $a, b \in \mathbf{B}^n$, $c_{n-1}, c_{-1} \in \mathbf{B}$ and $s \in \mathbf{B}^n$,
such that $\langle c_{n-1}, s \rangle = \langle a \rangle + \langle b \rangle + c_{-1}$.

Then:

1. $[a]_2 + [b]_2 + c_{-1} \notin R_n \Leftrightarrow (a_{n-1} = b_{n-1} \neq s_{n-1})$
2. $[a]_2 + [b]_2 + c_{-1} \in R_n \Rightarrow [a]_2 + [b]_2 + c_{-1} = [s]_2$

Proof of 1. via case distinction $[a]_2, [b]_2$ both positive, both negative,
 $[a]_2$ negative $[b]_2$ positive, $[a]_2$ positive $[b]_2$ negative.

Proof of 2. follows from the previous theorem.

Alternatively one can use the following overflow test:

$$[a]_2 + [b]_2 + c_{-1} \notin R_n \Leftrightarrow c_{n-1} \neq c_{n-2}$$

Carry-lookahead adder

Adder with
linear cost and logarithmic depth!

Approach: Fast precomputation of the carries c_i .

If the carries c_i are known, then s_i is simply $a_i \oplus b_i \oplus c_{i-1}$.

Computation of c_i via **parallel prefix computation**.

Parallel prefix computation

Definition:

Let M be a set and $\circ : M \times M \rightarrow M$ an associative operation.

The **parallel prefix sum** $PP^n : M^n \rightarrow M^n$ is defined as follows:

$$PP^n (x_{n-1}, \dots, x_0) = (x_{n-1} \circ x_{n-2} \dots \circ x_0, \dots, x_1 \circ x_0, x_0)$$

Parallel prefix computation:

Recursive construction: Base case

$$PP^n(x_{n-1}, \dots, x_0) = (x_{n-1} \circ x_{n-2} \dots \circ x_0, \dots, x_1 \circ x_0, x_0)$$

Base case: $PP^1(x_0) = (x_0)$

x_0

y_0

$=$

x_0


PP^1

y_0

Parallel prefix computation:

PP^n based on $PP^{n/2}$
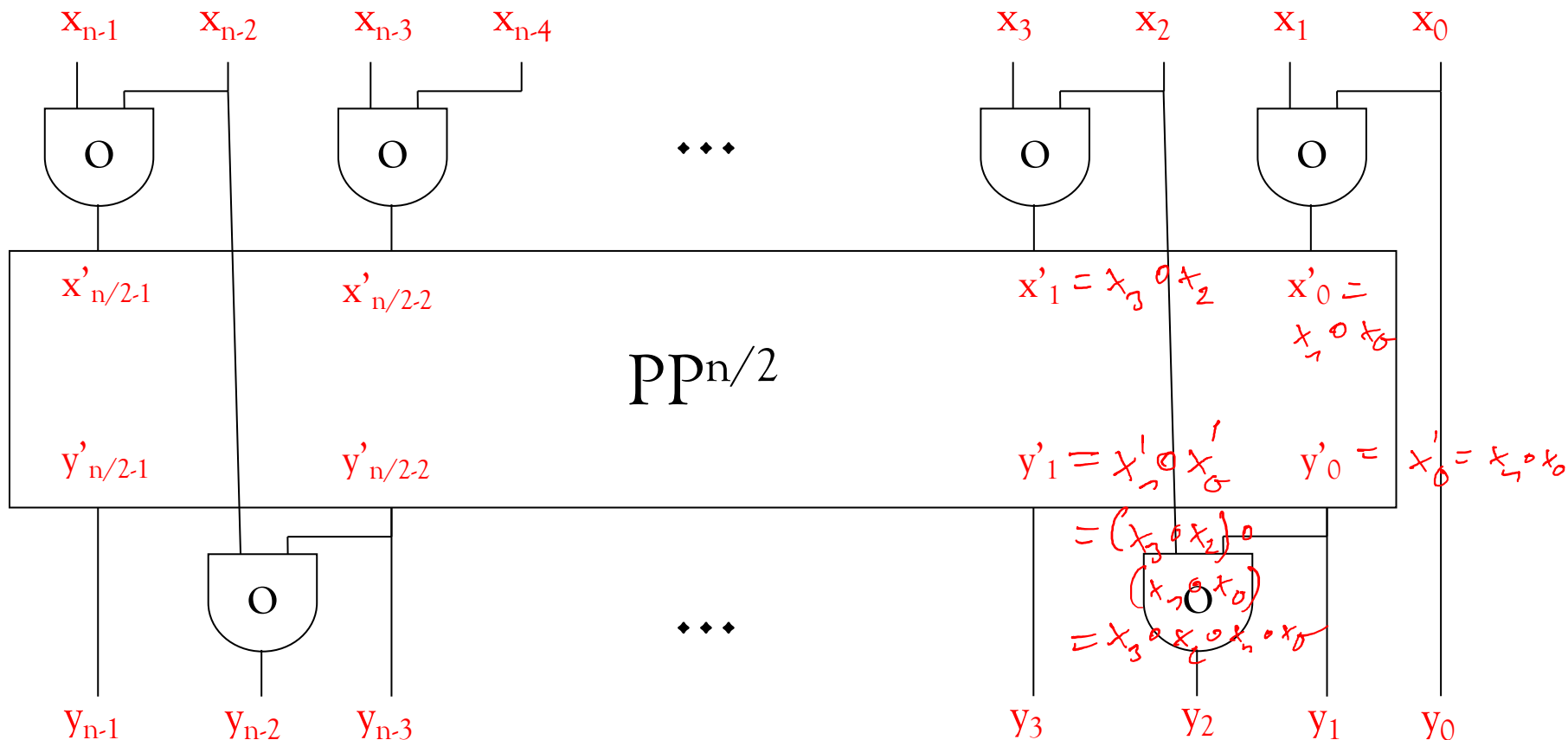
$$PP^n(x_{n-1}, \dots, x_0) = (x_{n-1} \circ x_{n-2} \dots \circ x_0, x_{n-2} \circ x_{n-3} \circ \dots \circ x_0, \dots, x_0)$$



Parallel prefix computation :

Correctness (for $n = 2^i$)

Induction base ($i=0, n=1$): ✓

Induction step ($n/2 \rightarrow n$):

Inductive hypothesis: $y'_i = x'_i \circ x'_{i-1} \circ \dots \circ x'_0$

For the *odd* outputs we have:

$$\begin{aligned} y_{2i+1} &= y'_i = x'_i \circ x'_{i-1} \circ \dots \circ x'_0 && \text{(inductive hypothesis)} \\ &= (x_{2i+1} \circ x_{2i}) \circ \dots \circ (x_1 \circ x_0) \\ &= x_{2i+1} \circ x_{2i} \circ \dots \circ x_1 \circ x_0 && \text{(associativity)} \end{aligned}$$

For the *even* outputs (except $i = 0$) we have:

$$\begin{aligned} y_{2i} &= x_{2i} \circ y'_{i-1} = x_{2i} \circ (x'_{i-1} \circ \dots \circ x'_0) && \text{(inductive hypothesis)} \\ &= x_{2i} \circ ((x_{2i-1} \circ x_{2i-2}) \circ \dots \circ (x_1 \circ x_0)) \\ &= x_{2i} \circ x_{2i-1} \circ \dots \circ x_1 \circ x_0 && \text{(associativity)} \end{aligned}$$

Cost of parallel prefix computation (for $n = 2^i$)

$$\text{Cost: } C(\text{PP}^n) < 2n \cdot C(o)$$

Proof by induction over i :

- $i=0, n=1$:

$$C(\text{PP}^1) = 0 < 2 \cdot C(o)$$

- $n \rightarrow 2n$:

$$\begin{aligned} C(\text{PP}^{2n}) &= C(\text{PP}^n) + (2n-1) \cdot C(o) \\ &< 2n \cdot C(o) + (2n-1) \cdot C(o) && \text{(I.H.)} \\ &< 2(2n) \cdot C(o) \end{aligned}$$

Depth of parallel prefix computation(for $n = 2^i$)

$$\text{Depth: } \text{depth}(\text{PP}^n) < (2 \cdot \log_2 n) \cdot \text{depth}(\text{o})$$

Proof by induction over i :

- $i=0, n=1$: $\text{depth}(\text{PP}^1) = 0 < 2$
 $= (2 \cdot \log_2 2) \cdot \text{depth}(\text{o})$
- $n \rightarrow 2n$: $\text{depth}(\text{PP}^{2n}) = \text{depth}(\text{PP}^n) + 2 \cdot \text{depth}(\text{o})$
 $\leq^{(\text{I.H.})} (2 \cdot \log n + 2) \cdot \text{depth}(\text{o})$
 $= (2 \cdot (\log n + 1)) \cdot \text{depth}(\text{o})$
 $= (2 \cdot \log (2n)) \cdot \text{depth}(\text{o})$

Back to the adder:

Precomputation of the carries

Distinguish **generated** and **propagated** carries:

$$\begin{array}{ccccccc}
 a_{n-1} & \dots & a_j & \dots & a_i & \dots & a_0 \\
 b_{n-1} & \dots & b_j & \dots & b_i & \dots & b_0 \\
 \dots & \underline{c_j} & c_{j-1} & \dots & \underline{\underline{c_{i-1}}} & \dots & c_1
 \end{array}$$

$$\begin{array}{cccc}
 j & & i & \\
 1 & 1 & 1 & 1 \\
 0 & 0 & 0 & 0 \\
 c_j & & c_{i-1} &
 \end{array}
 \quad
 \boxed{p_{j,i}}$$

$$\begin{array}{cccc}
 1 & 0 & 1 & 1 \\
 0 & 0 & 0 & 1 \\
 c_j & & c_{i-1} &
 \end{array}
 \quad
 \cancel{\boxed{p_{j,i}}} \quad \cancel{\boxed{g_{j,i}}}$$

Generated carry $g_{j,i}$ from i to j :

$c_j = 1$ independently of c_{i-1} .

Propagated carry $p_{j,i}$ from i to j :

$c_j = 1$ if and only if also $c_{i-1} = 1$

Examples?

$$\begin{array}{cccc}
 1 & 0 & 1 & 1 \\
 0 & 1 & 1 & 0 \\
 c_j & & c_{i-1} &
 \end{array}
 \quad
 \boxed{g_{j,i}}$$

Properties of generated and propagated carries

Carry c_j is obtained as follows:

$$c_j = g_{j,0} + p_{j,0} \cdot c_{-1}$$

For $i = j$ we have:

$$p_{i,i} = a_i \otimes b_i,$$

$$g_{i,i} = a_i \cdot b_i.$$

	c_{i-1}	c_i
p_i	0	1
g_i	1	0

For $i \neq j$ with $i \leq k < j$ we have:

$$g_{j,i} = g_{j,k+1} + p_{j,k+1} \cdot g_{k,i},$$

$$p_{j,i} = p_{j,k+1} \cdot p_{k,i}.$$

	c_{i-1}	c_i
p_i	0	1
g_i	1	0

Associative operator for the computation of $g_{j,i}$ and $p_{j,i}$

Define operator \circ as follows

$$(g, p) \circ (g', p') = (g + p \cdot g', p \cdot p'),$$

so that

$$(g_{j,i}, p_{j,i}) = (g_{j,k+1}, p_{j,k+1}) \circ (g_{k,i}, p_{k,i}).$$


Then we have:

$$(g_{j,0}, p_{j,0}) = (g_{j,j}, p_{j,j}) \circ \dots \circ (g_{1,1}, p_{1,1}) \circ (g_{0,0}, p_{0,0})$$

The operator \circ is associative.

→ Parallel prefix computation to determine $(g_{j,0}, p_{j,0})$

Carry-lookahead adder

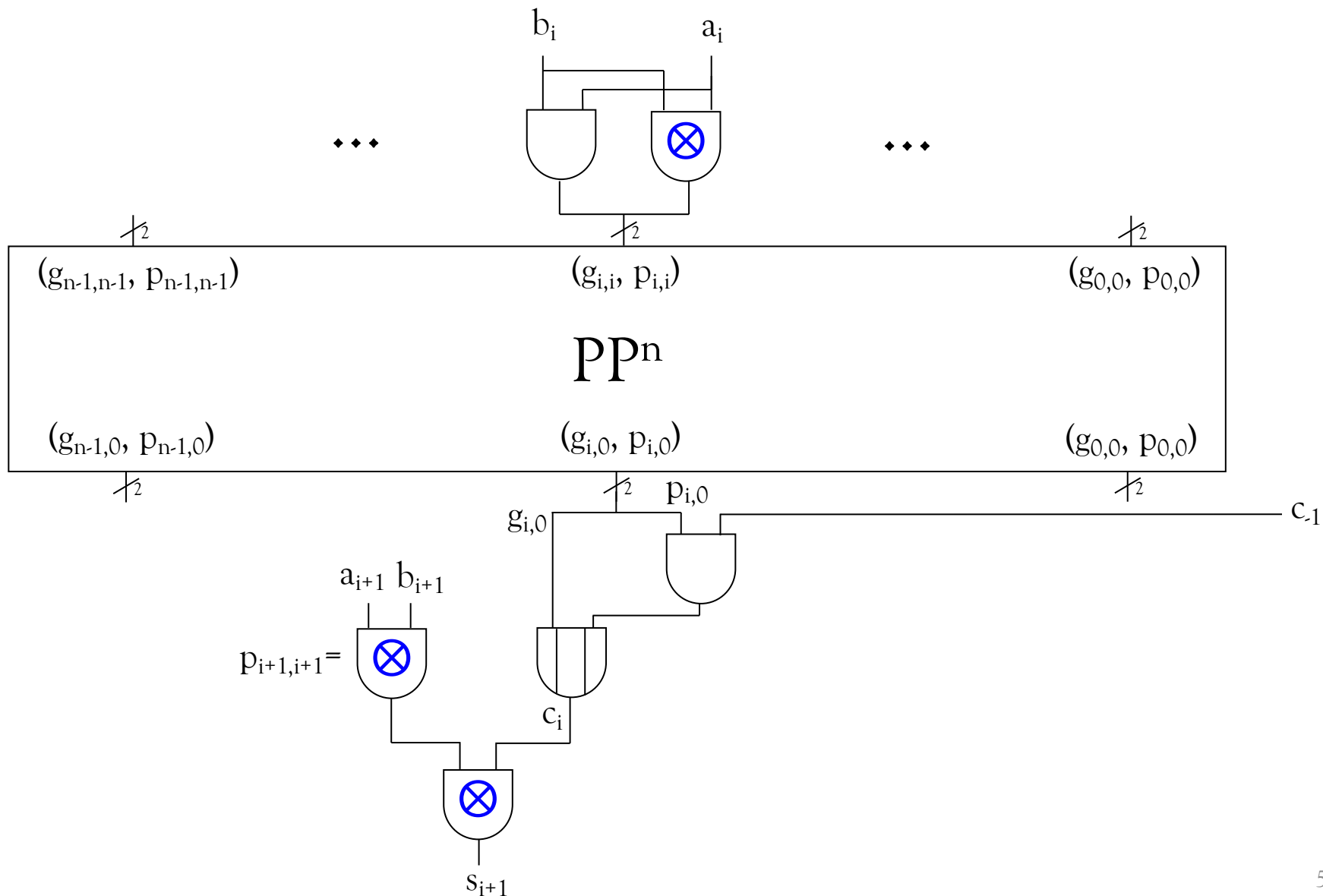

Cost and depth of the CLA^n

$$\begin{aligned}\text{Cost: } C(\text{CLA}^n) &= C(\text{PP}^n) + 5n \\ &< 2n \cdot C(o) + 5n \\ &= 11n\end{aligned}$$

$$\begin{aligned}\text{Depth: } \text{depth}(\text{CLA}^n) &= \text{depth}(\text{PP}^n) + 4 \\ &\leq (2 \cdot \log n - 1) \cdot \text{depth}(o) + 4 \\ &= 4 \cdot \log n + 2\end{aligned}$$

Summary:

Circuits and their complexity

	Half adder	Full adder	Ripple-carry adder	Conditional- sum adder	Carry-lookahead adder
Cost	2	5	$5 \cdot n$	$10 \cdot n^{\log 3} - 3 \cdot n - 2$	$11 \cdot n$
Depth	1	3	$3 + 2 \cdot (n - 1)$	$3 \cdot \log n + 3$	$4 \cdot \log n + 2$

	Incrementer	Multiplexer	arbitrary n-bit adder	Parallel prefix computation
Cost	$2 \cdot n$	$3 \cdot n + 1$	$\geq 2 \cdot n$	$< 2 \cdot n \cdot C(o)$
Depth	n	3	$\geq \log n + 1$	$(2 \cdot \log n - 1) \cdot \text{depth}(o)$